

Fundamentals of Computer Systems

A Multicycle MIPS Processor




Stephen A. Edwards

Columbia University

Summer 2016


Illustrations Copyright © 2007 Elsevier

State Elements

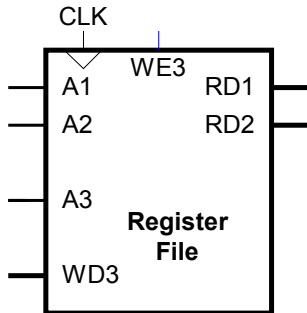  


Multicycle Datapath

Fetch instruction from memory

 


Multicycle Datapath

Read source operands from register file

 


Multicycle Datapath

Sign-extend the immediate

 


Multicycle Datapath

Add base address to offset

 


Multicycle Datapath

Load data from memory

 


Multicycle Datapath

Write data back to register file

 


Multicycle Datapath

Add 4 to PC

 


Multicycle Datapath

For sw: Write register data to memory

 


Multicycle Datapath

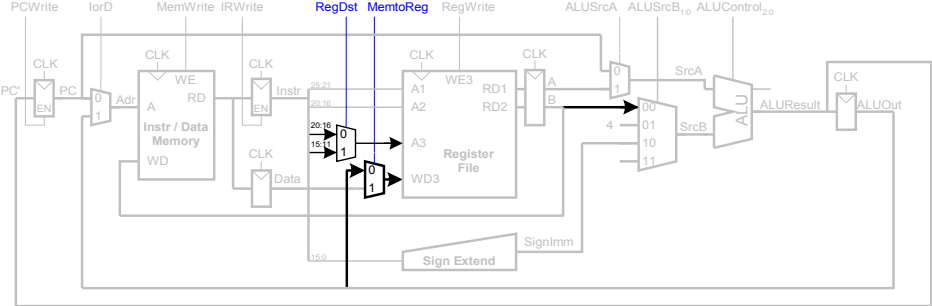For R-type instructions: Write ALU result to registers




Multicycle Datapath

For bne: Add immediate to PC

 


Multicycle Datapath

Add Controller

 


Controller Internals

 



Controller Behavior




Fetch

 


Controller Behavior

  


Controller Behavior

 


Controller Behavior

 


Controller Behavior

 


Controller Behavior

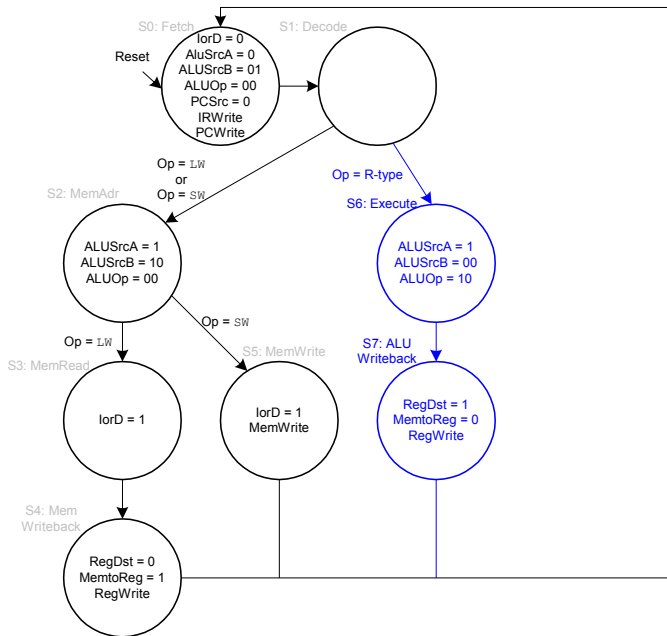

Controller Behavior

 


Controller Behavior

 


Controller Behavior

 
Additional circuitry for the jump instruction



Controller Behavior

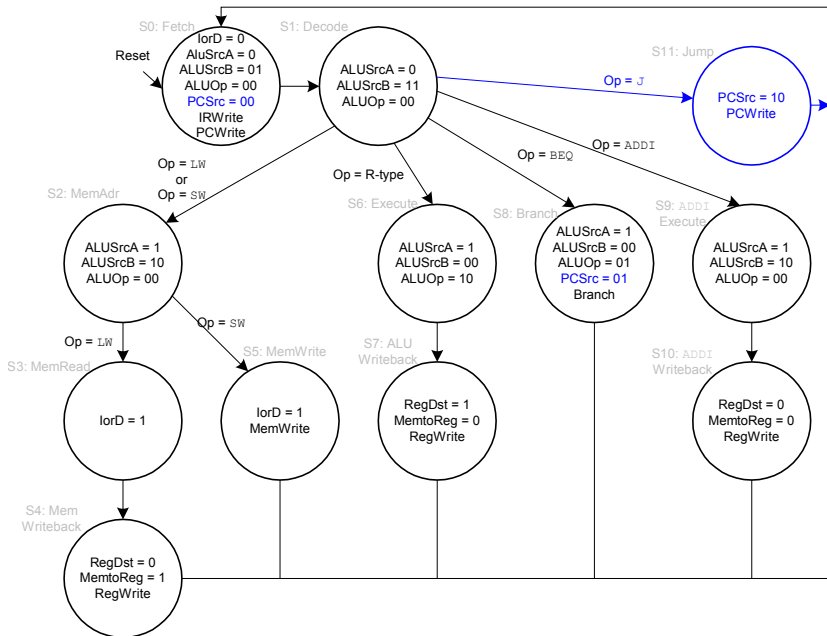


Multicycle Critical Path

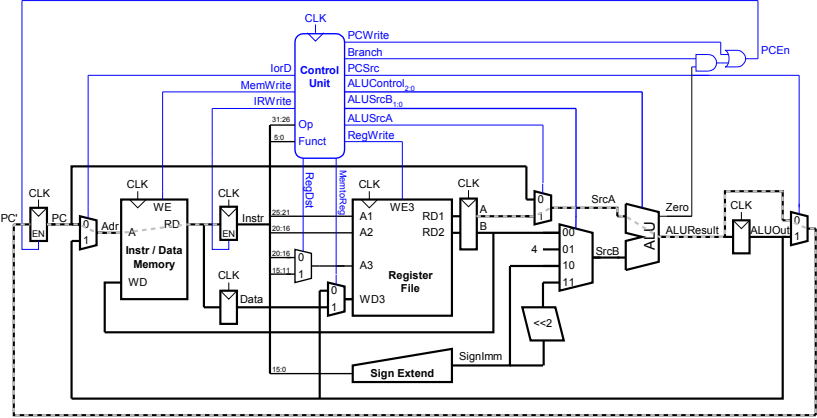

Two hypotheses: Reading memory or going through the ALU

Multicycle Clock Period

Element	Delay
Register clk-to-Q	t_{pcq-PC} 30 ps
Register setup	t_{setup} 20
Multiplexer	t_{mux} 25
ALU	t_{ALU} 200
Memory Read	t_{mem} 250
Register file read	t_{RFread} 150
Register file setup	$t_{RFsetup}$ 20

 

$$\begin{aligned}T_C &= t_{pcq-PC} + t_{mux} + \max\{t_{ALU} + t_{mux}, t_{mem}\} + t_{RFsetup} \\&= (30 + 25 + \max\{200 + 25, 250\} + 20) \text{ ps} \\&= 325 \text{ ps} \\&= 3.08 \text{ GHz}\end{aligned}$$

vs. 925 ps for our single-cycle processor

Execution Time for Our Multi-Cycle Processor

For a 100 billion-instruction task on our multi-cycle processor, each instruction takes 4.12 cycles on average. With a 325 ps clock period,

$$\begin{aligned}\frac{\text{Seconds}}{\text{Program}} &= \frac{\text{Instructions}}{\text{Program}} \times \frac{\text{Clock Cycles}}{\text{Instruction}} \times \frac{\text{Seconds}}{\text{Clock Cycle}} \\ &= 100 \times 10^9 \times 4.12 \times 325 \text{ ps} \\ &= 133.9 \text{ seconds}\end{aligned}$$

vs. 92.5 seconds for our single-cycle processor.