

---

Complete the following problems. Be sure to show your work for partial credit.

1. An  $m$ -bit *thermometer code* for the number  $k$  consists of  $k$  1's in the least significant bit positions and  $m - k$  0's in all the more significant bit positions. A *binary-to-thermometer converter* has  $n$  inputs and  $2^n - 1$  outputs. It produces a  $2^n - 1$  bit thermometer code for the number specified by the input. For example, if the input is 110, the output should be 0111111. Design a 3:7 binary-to-thermometer code converter. Specify your design in the way that seems most natural to you, using a block diagram, schematic, or boolean expression (or some combination of these).
2. Design a modified priority encoder that receives an 8-bit input,  $A_{7:0}$ , and produces two 3-bit outputs,  $Y_{2:0}$  and  $Z_{2:0}$  and two 1-bit outputs,  $v$  and  $w$ .  $v$  should be TRUE if there are one or more TRUE bits on the input.  $Y$  indicates the most significant bit of the input that is TRUE.  $w$  should be TRUE if there are two or more TRUE bits on the input.  $Z$  indicates the second most significant bit of the input that is TRUE. Specify your design in the way that seems most natural to you, using a block diagram, schematic, or boolean expression (or some combination of these).
3. Design a full adder module with data inputs  $A$  and  $B$ , carry input  $C_{in}$ , sum output  $S$ , and carry output  $C_{out}$ .
  - (a) Using two half adder modules.
  - (b) Using a 3:8 decoder and NAND gates.
  - (c) Using a four input, 2-bit multiplexer.
4. Design a 4-bit comparator. This comparator takes two 4-bit operands,  $A_{3:0}$  and  $B_{3:0}$  and has three outputs  $L$ ,  $E$ , and  $G$ . The outputs are true when  $A < B$ ,  $A = B$ , and  $A > B$  respectively. Define a single-bit comparator module and show
  - (a) how they are wired together to form a 4-bit comparator, and
  - (b) boolean expressions describing the behavior of this module