

CSEE 3827: Fundamentals of Computer Systems


Lecture 12

March 2, 2009

Martha Kim


martha@cs.columbia.edu

Moore machine

 

a circuit in which the output depends only on the current state


Mealy machine

 


a circuit in which the outputs depend on the inputs as well as the current state

FSM timing characteristics

MEALY

 


MOORE

 


Flip-flop timing requirements

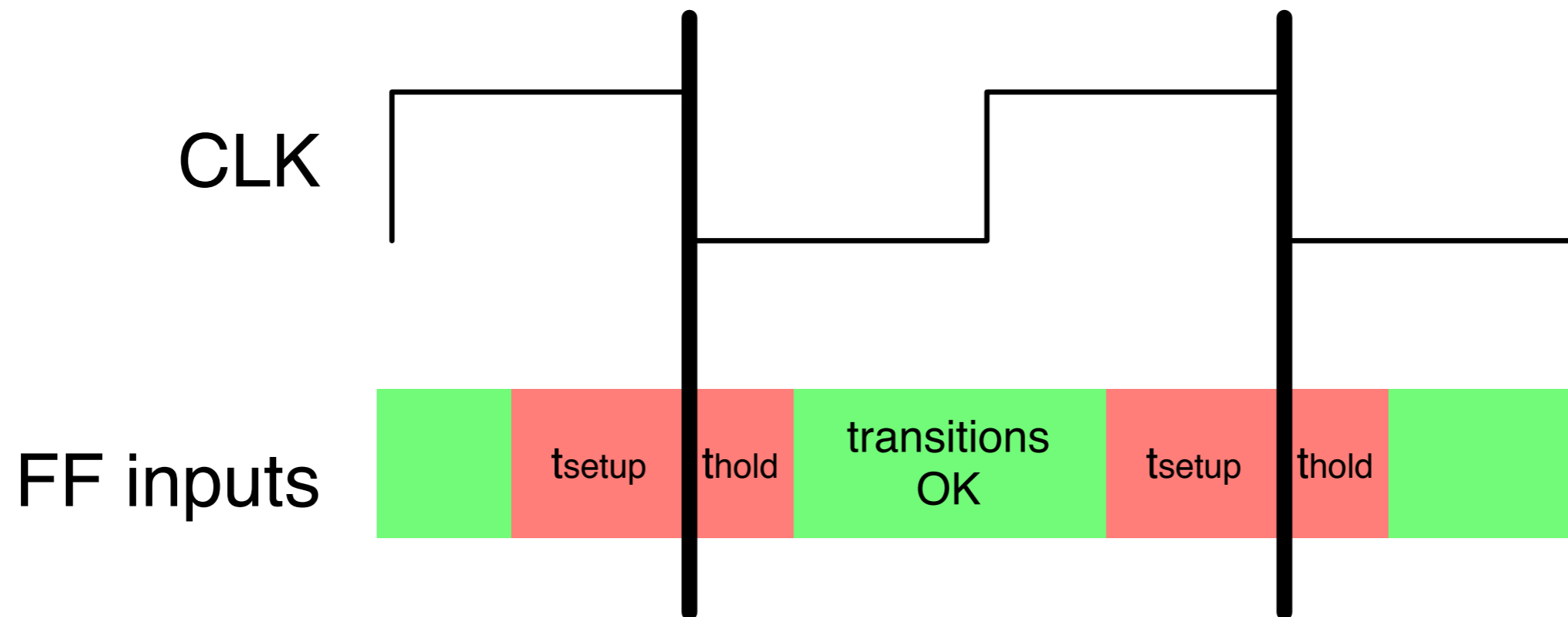- Flip-flops sample their inputs at each rising or falling clock edge
- The input data must be held stable for some time before and after the sample




A Mealy or Moore circuit?

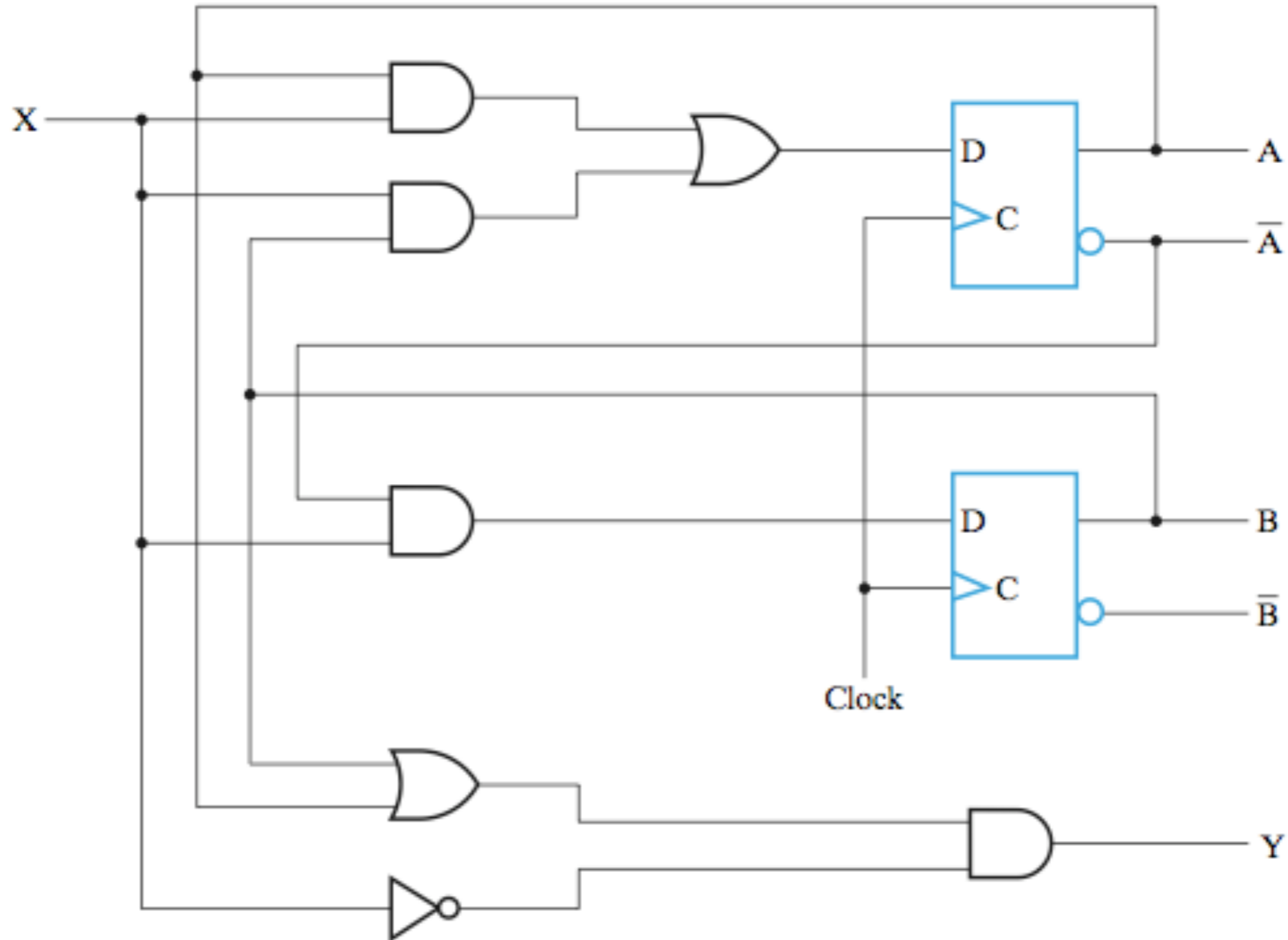

© 2008 Pearson Education, Inc.
M. Morris Mano & Charles R. Kime
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

An example Moore circuit

5-16

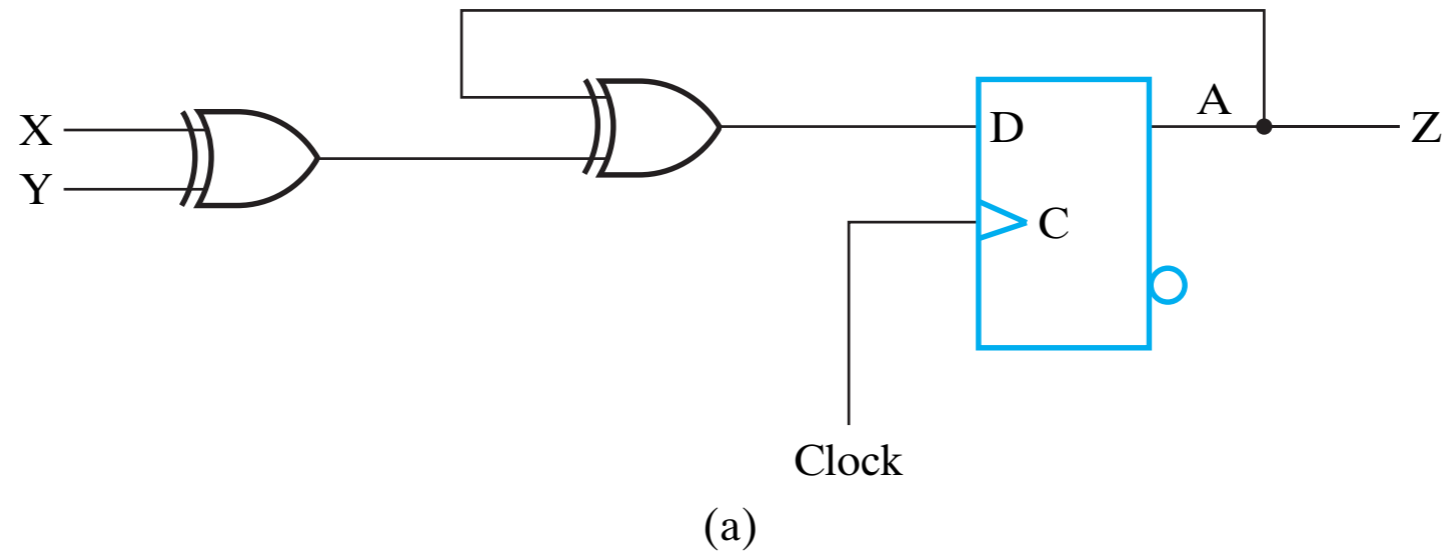

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(b) State table

In class exercise: design a vending machine

- This vending machine will dispense a soda after the user has entered \$.15
- Inputs: N, D (nickel, dime, quarter inserted)
- Output: R (release soda)

FSM design and implementation techniques

Unused states: *extra state encodings (e.g., using 3 FFs to represent 6 states leaves 2 unused states) can be treated as “don’t care” values and used to simplify the combinational logic*

This reduces combinational logic, which means a faster clock.

State minimization: *two states are equivalent if they transition to the same or equivalent states on the same inputs while producing the same outputs*

This can reduce the number of flip-flops.