

CSEE 3827: Fundamentals of Computer Systems

Lecture 2

January 26, 2009

Martha Kim

mak2191@columbia.edu

Agenda

- TA office hours
- Boolean algebra
- Logic gates
- Circuit fabrication

TA Office Hours

TA Room, first floor of Mudd (see: <http://ta.cs.columbia.edu/tamap.shtml>)

Roopa Kakarlapudi Tuesdays 5-6:30PM

Harsh Parekh Mondays 11-12:20PM; Tuesdays 3:30-5PM

Nishant Shah Wednesdays 10-11:30AM

Boolean Logic

- Binary digits (or bits) have two values: $\{1,0\}$
- All logical functions can be implemented in terms of three logical operations:

NOT

x	\bar{x}
0	1
1	0

AND

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

Boolean Logic 2

- Precedence rules just like decimal system
- Implied precedence: NOT > AND > OR
- Use parentheses as necessary

$$AB + C = (AB) + C$$

$$(\overline{A} + B)C = ((\overline{A}) + B)C$$

Boolean Logic: Example

D	X	A	$L = \overline{DX} + A$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Boolean Logic: Example

D	X	A	\bar{X}	$D\bar{X}$	$L = D\bar{X} + A$
0	0	0	1	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	1	0	0	1

(M&K Table 2-2)

Boolean Logic: Example 2

X	Y	$XY + \overline{XY}$
0	0	
0	1	
1	0	
1	1	

Boolean Logic: Example 2

X	Y	\bar{X}	\bar{Y}	XY	\overline{XY}	$XY + \overline{XY}$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

Boolean Algebra: Identities and Theorems

OR	AND	NOT	
$X+0 = X$	$X1 = X$		(identity)
$X+1 = 1$	$X0 = 0$		(null)
$X+X = X$	$XX = X$		(idempotent)
$X+\overline{X} = 1$	$X\overline{X} = 0$		(complementarity)
		$\overline{\overline{X}} = X$	(involution)
$X+Y = Y+X$	$XY = YX$		(commutativity)
$X+(Y+Z) = (X+Y)+Z$	$X(YZ) = (XY)Z$		(associativity)
$X(Y+Z) = XY + XZ$	$X+YZ = (X+Y)(X+Z)$		(distributive)
$\overline{X+Y} = \overline{X}\overline{Y}$	$\overline{XY} = \overline{X} + \overline{Y}$		(DeMorgan's theorem)

Boolean Algebra: Example

Simplify this equation using algebraic manipulation.

$$F = \overline{X}YZ + \overline{X}Y\overline{Z} + XZ$$

Boolean Algebra: Example

Simplify this equation using algebraic manipulation.

$$F = \overline{X}YZ + \overline{X}Y\overline{Z} + XZ$$

$$\overline{X}Y(Z + \overline{Z}) + XZ \quad (\text{by reverse distribution})$$

$$\overline{X}Y1 + XZ \quad (\text{by complementarity})$$

$$\overline{X}Y + XZ \quad (\text{by identity})$$

Boolean Algebra: Example 2

Find the complement of F.

$$F = A\bar{B} + \bar{A}B$$

$$\bar{F} =$$

Boolean Algebra: Example 2

Find the complement of F .

$$F = A\bar{B} + \bar{A}B$$

$$\bar{F} = \overline{A\bar{B} + \bar{A}B}$$

$$\overline{(A\bar{B}) (\bar{A}B)}$$

(by DeMorgan's)







$$(\bar{A} + B) (\overline{\bar{A} + \bar{B}})$$

(by DeMorgan's)

$$(\bar{A} + B) (A + \bar{B})$$




(by involution)

Boolean Algebra: Why?

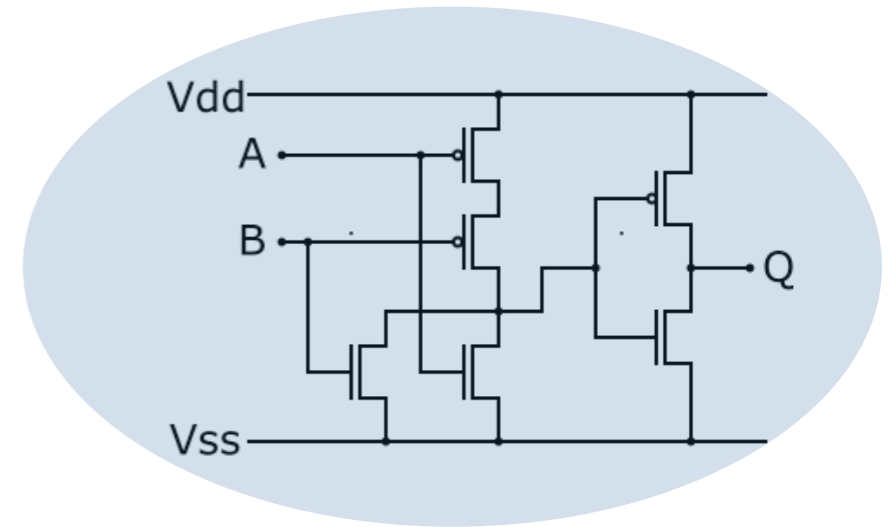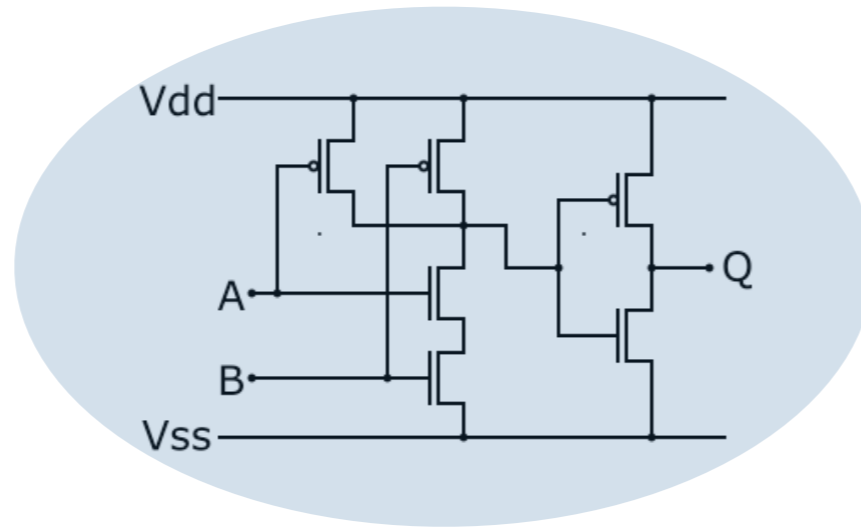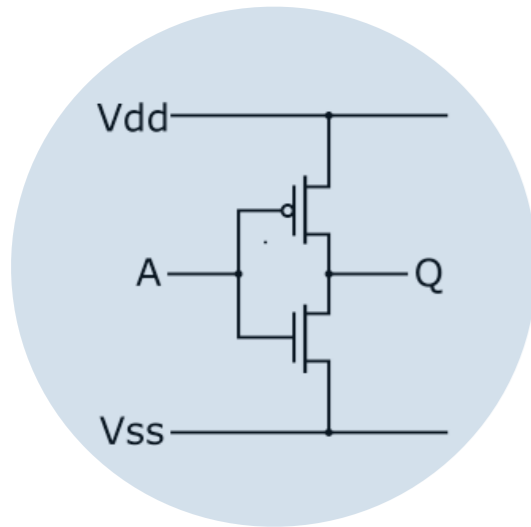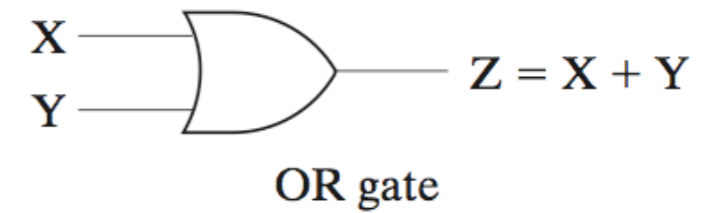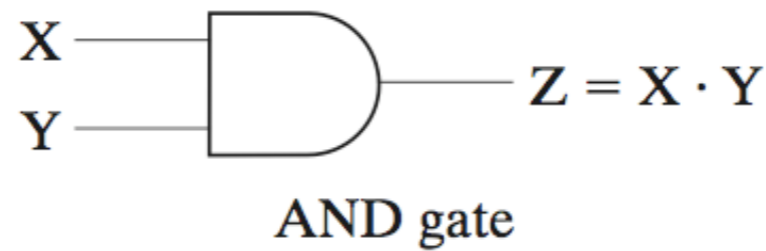
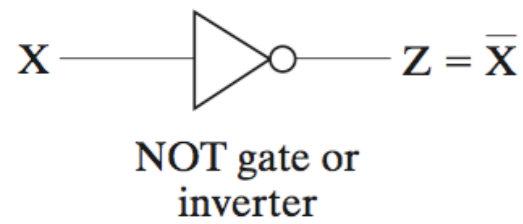


These circuits consume area, power, and time



Logic gate area

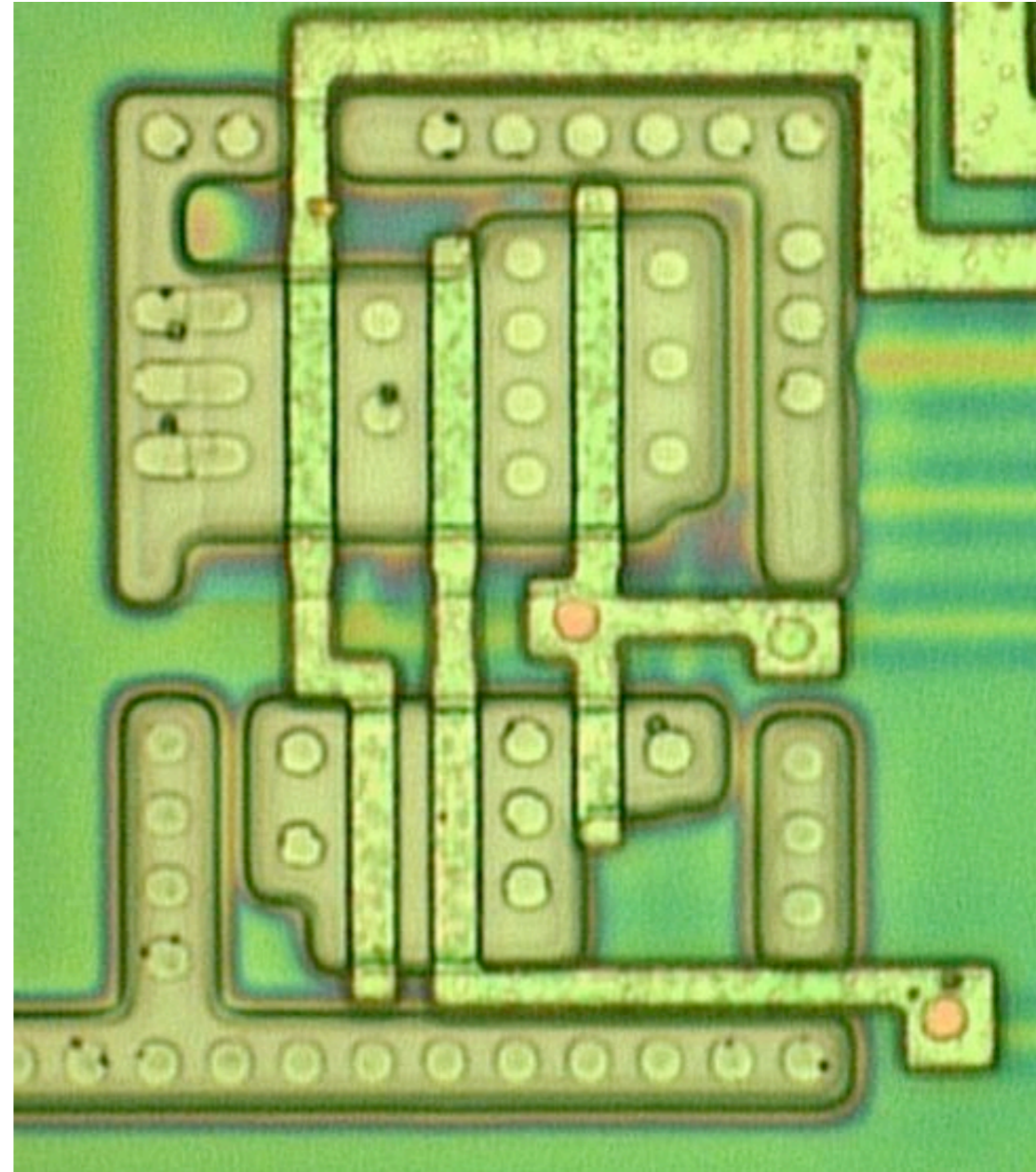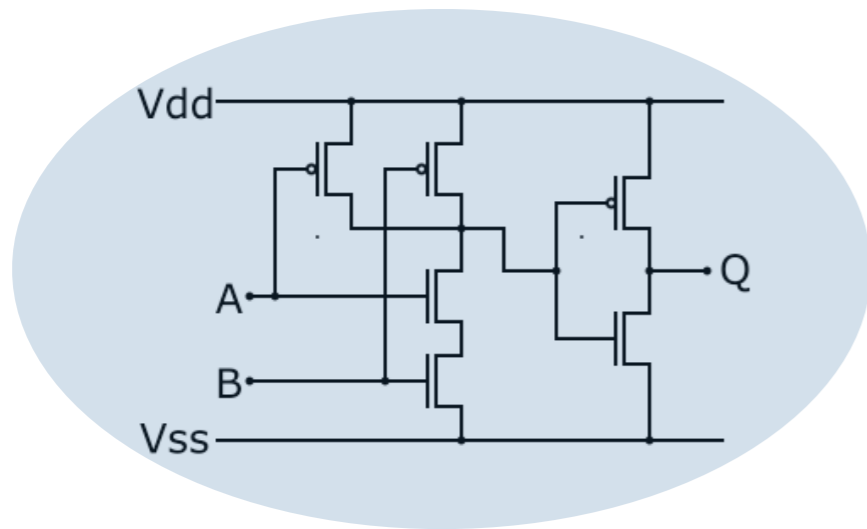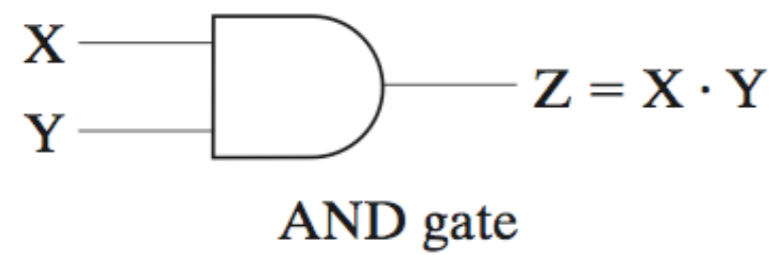

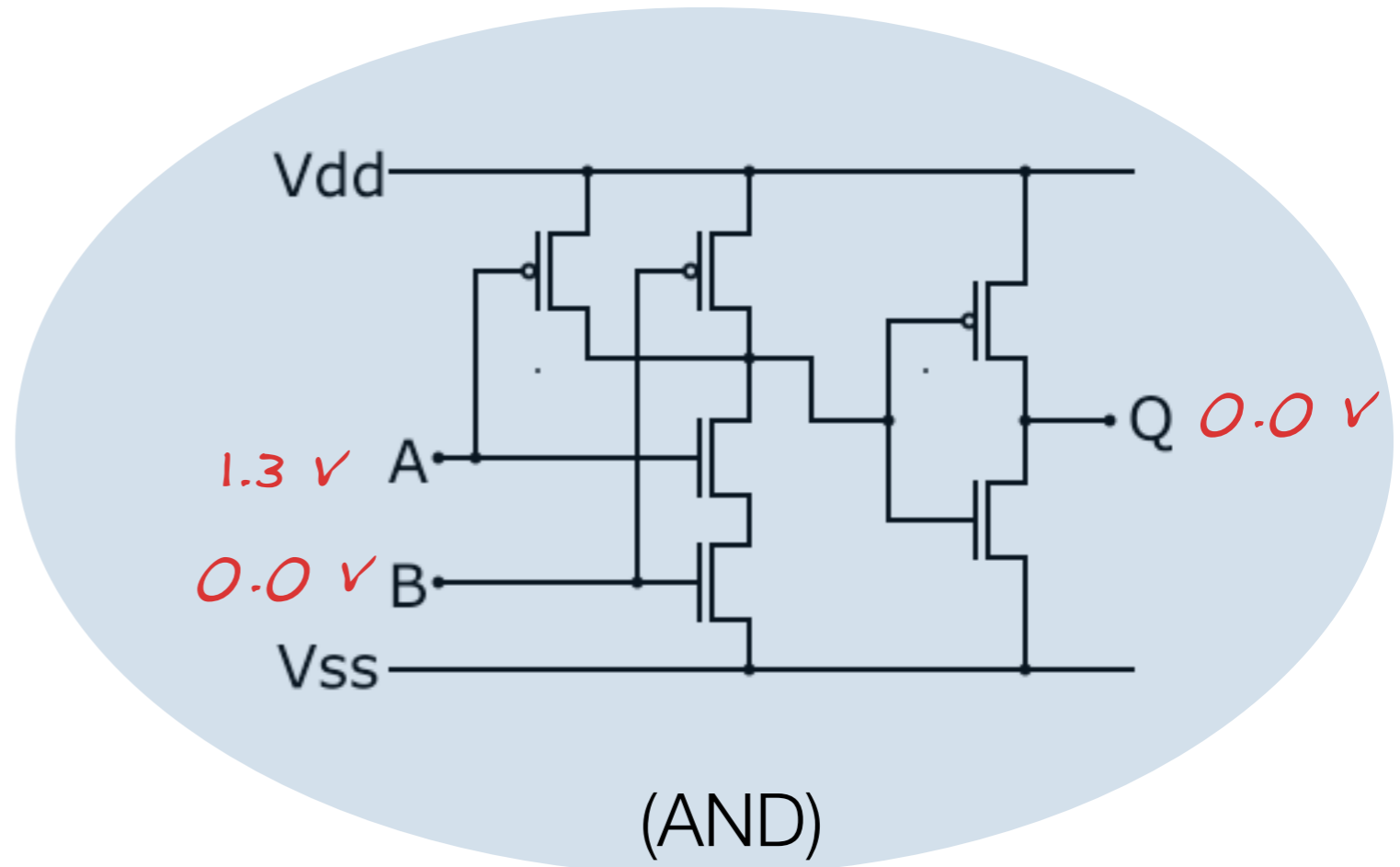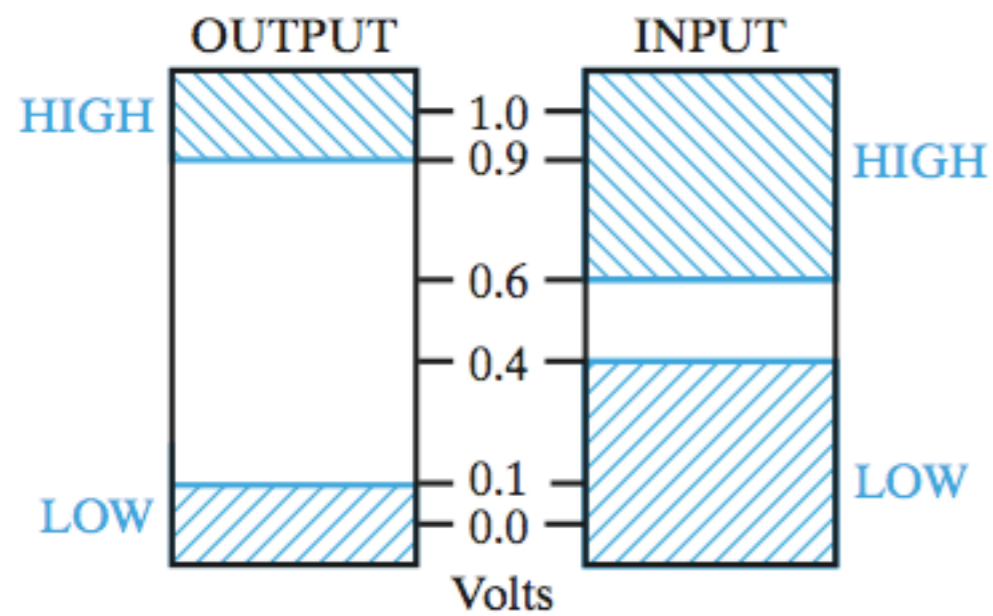Information signaled through voltage level




Idealized timing diagram of AND gate

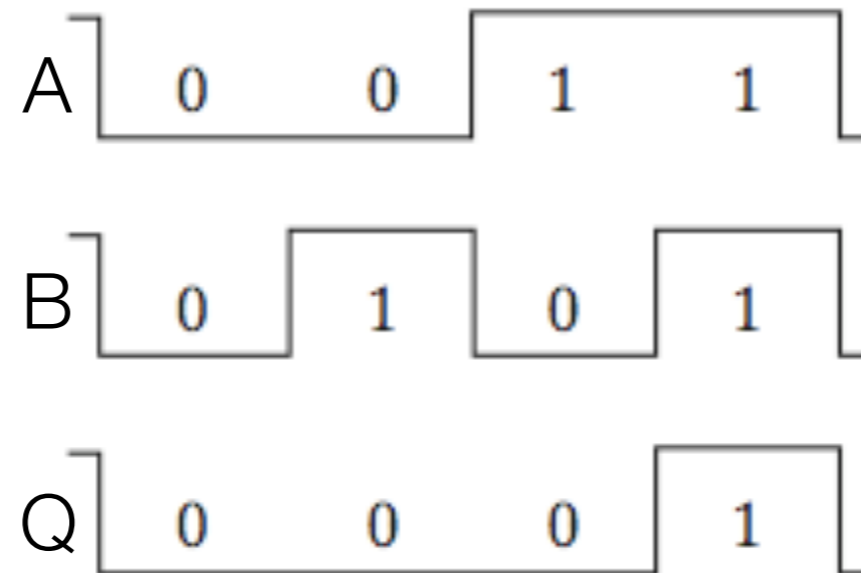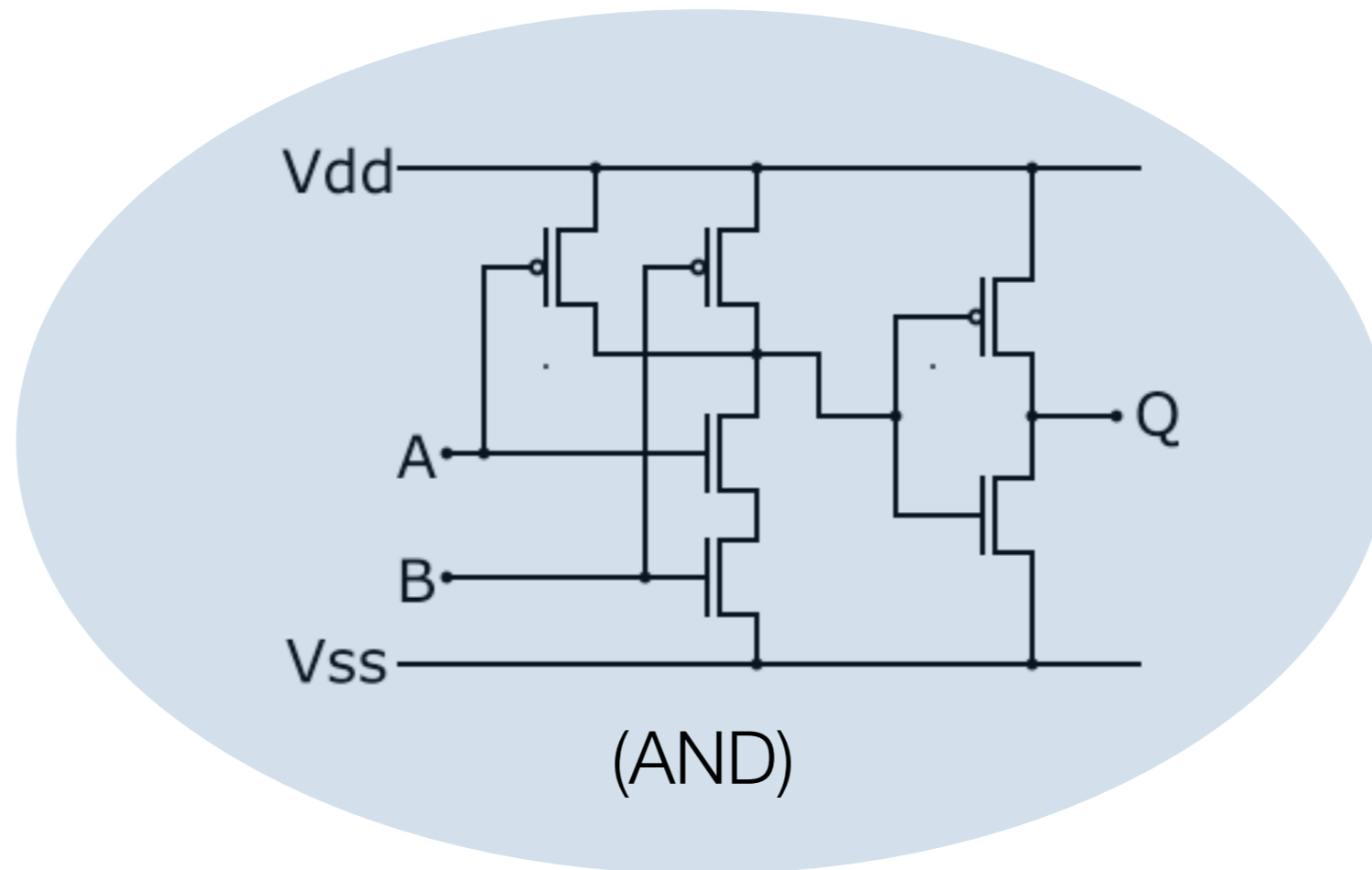


Actual signal timing has delays

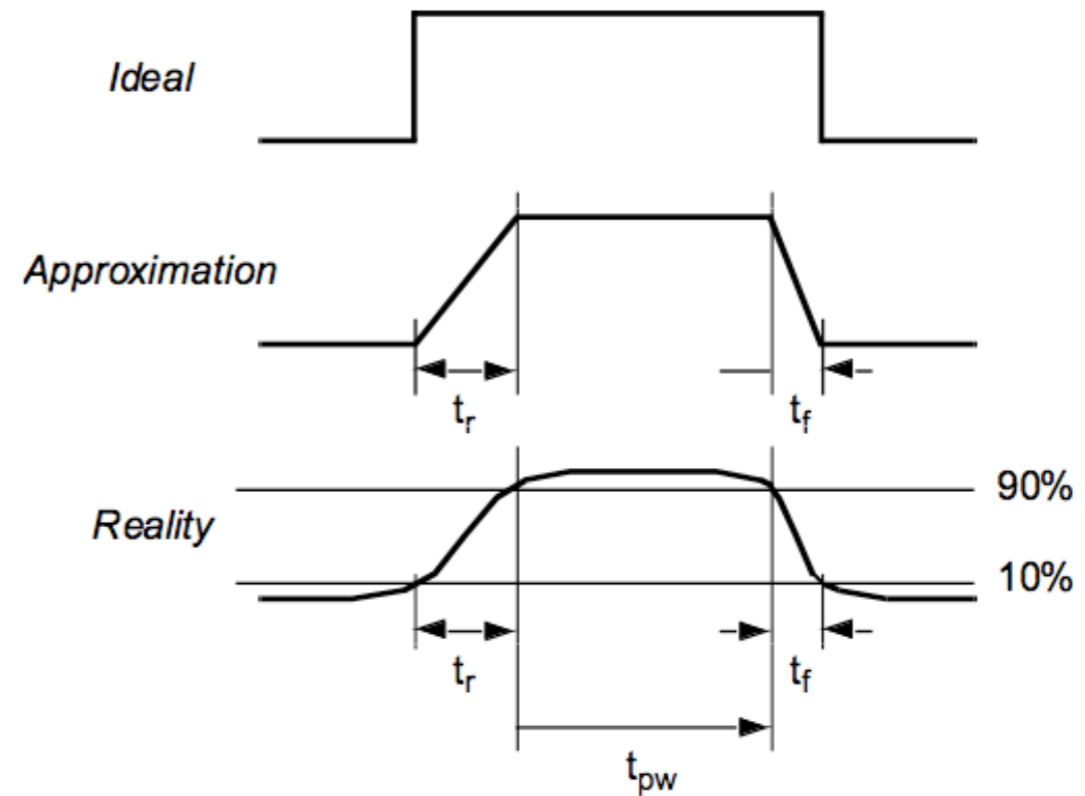- **transition time:** *time required for output to change (RC delay: ohms x farads = time)*



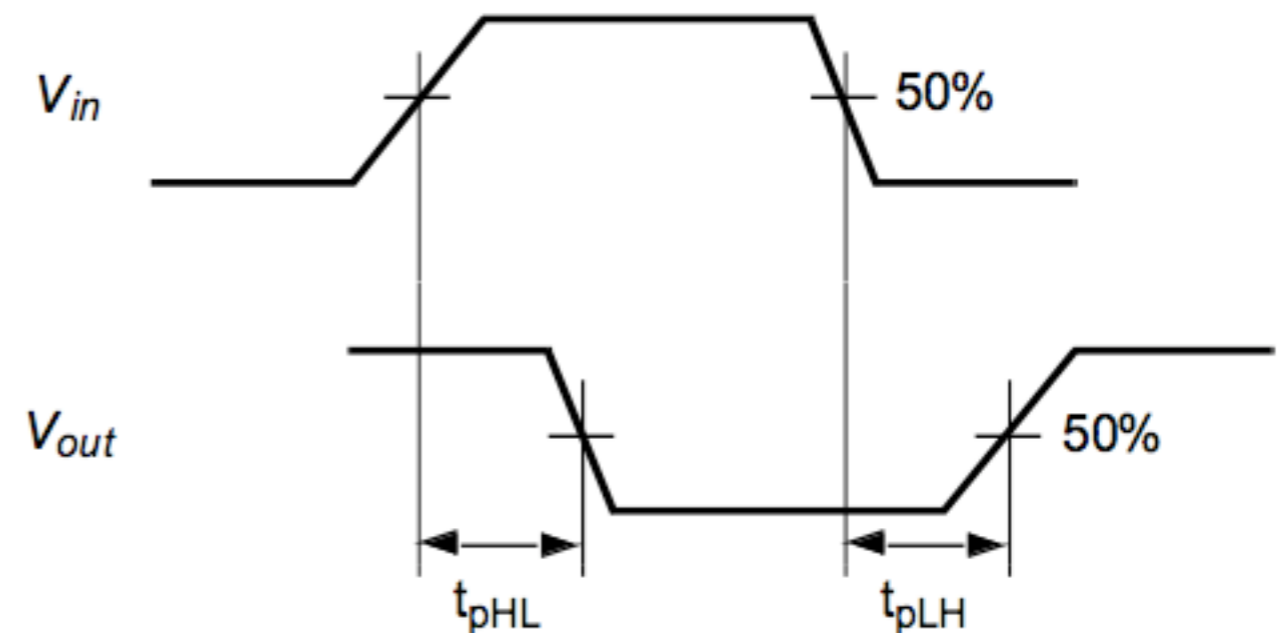- **propagation time:** *time from input change to output change*



Returning to boolean algebra...


$$F = \overline{X}YZ + \overline{X}Y\overline{Z} + XZ$$

$$\overline{X}Y(Z + \overline{Z}) + XZ \quad (\text{by reverse distribution})$$


$$\overline{X}Y1 + XZ \quad (\text{by complementarity})$$

$$\overline{X}Y + XZ \quad (\text{by identity})$$

Returning to boolean algebra...

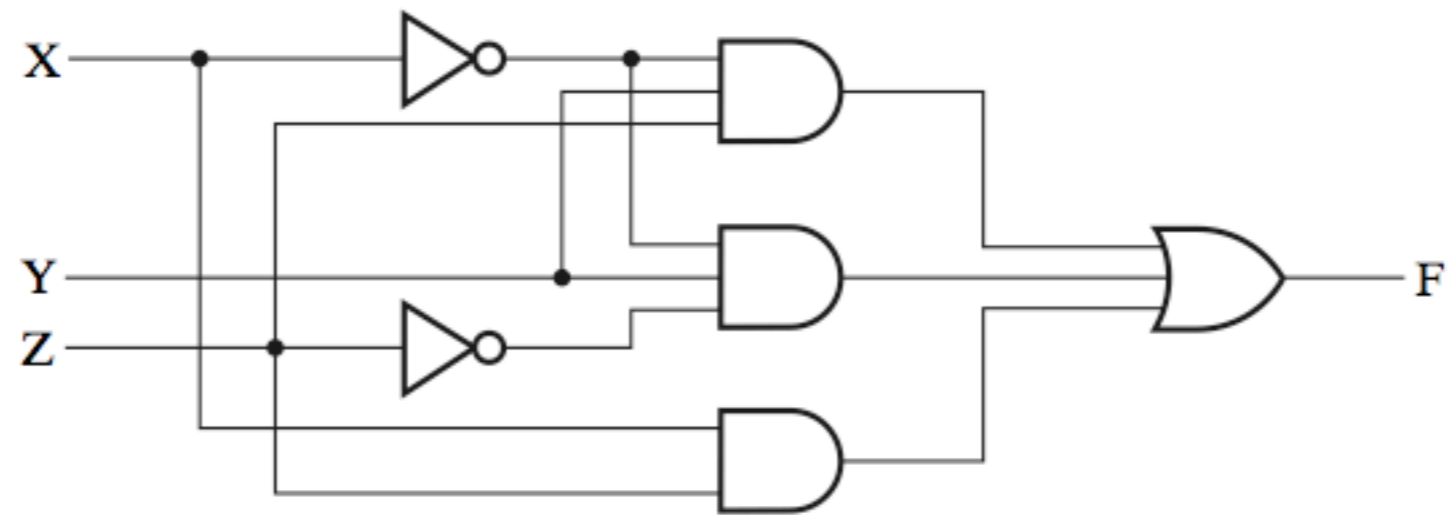

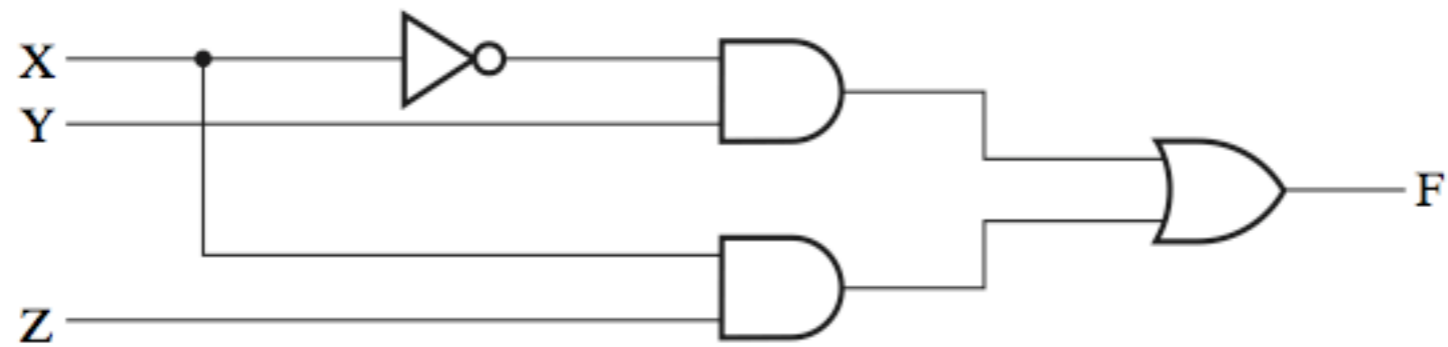(a) $F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$




(b) $F = \bar{X}Y + XZ$

Universal gates: NAND, NOR



x	y	$z = \overline{xy}$
0	0	1
0	1	1
1	0	1
1	1	0



x	y	$z = \overline{X+Y}$
0	0	1
0	1	0
1	0	0
1	1	0

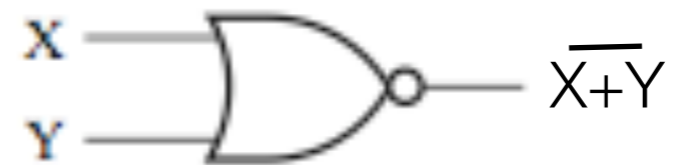

Universal how?

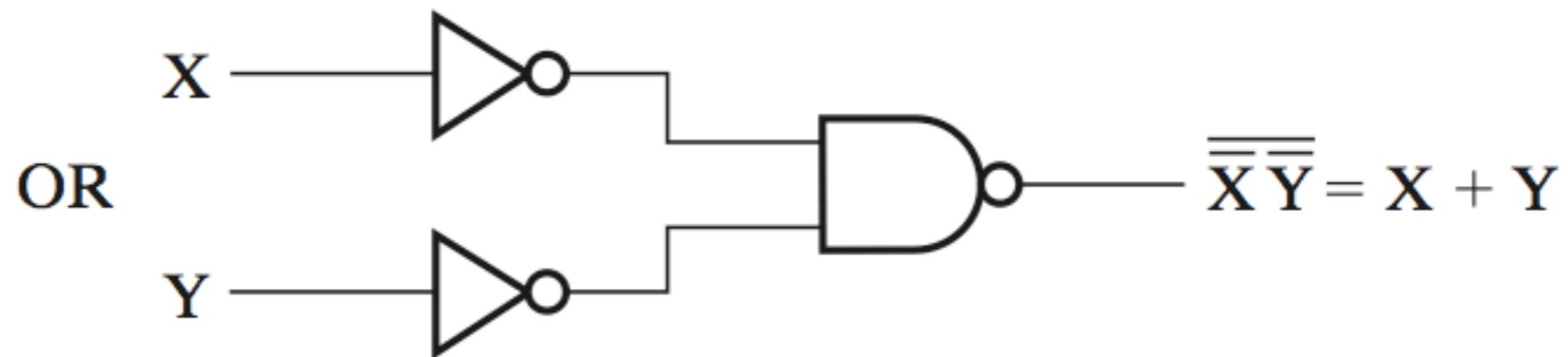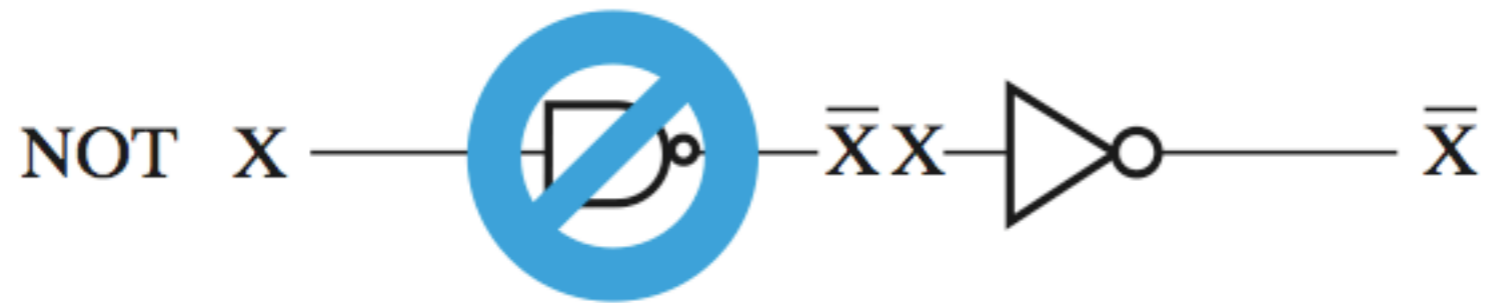

Boolean algebra practice 1

Prove that this boolean equation is true using algebraic manipulation.

$$1 = \bar{A}B + \bar{B}\bar{C} + AB + \bar{B}C$$

$$B(\bar{A} + A) + \bar{B}(\bar{C} + C) \quad (\text{by distribution})$$

$$B + \bar{B} \quad (\text{by complementarity})$$

$$1 \quad (\text{by complementarity})$$

Boolean algebra practice 2

Prove that this boolean equation is true using algebraic manipulation.

$$\bar{X} + Y = \bar{X}\bar{Y} + \bar{X}Y + XY$$

$$\bar{X}\bar{Y} + \bar{X}Y + \bar{X}Y + XY \quad (\text{by idempotence})$$

$$\bar{X}(\bar{Y} + Y) + Y(\bar{X} + X) \quad (\text{by distribution})$$

$$\bar{X}1 + Y1 \quad (\text{by null})$$

$$\bar{X} + Y \quad (\text{by identity})$$

Boolean algebra practice 3

Find the complement of F.

$$F = (\bar{V}W + X)Y + \bar{Z}$$

$$\bar{F} = \overline{(\bar{V}W + X)Y + \bar{Z}}$$

$$\overline{((\bar{V}W + X)Y)\bar{Z}}$$

(by DeMorgan's)

$$\overline{((\bar{V}W + X) + \bar{Y})Z}$$

(by DeMorgan's & involution)

$$(\overline{\bar{V}W} \bar{X} + \bar{Y})Z$$

(by DeMorgan's)

$$((\bar{V} + \bar{W})\bar{X} + \bar{Y})Z$$

(by DeMorgan's)


$$((V + W)\bar{X} + \bar{Y})Z$$

(by null)


Integrated circuit fabrication




raw silicon

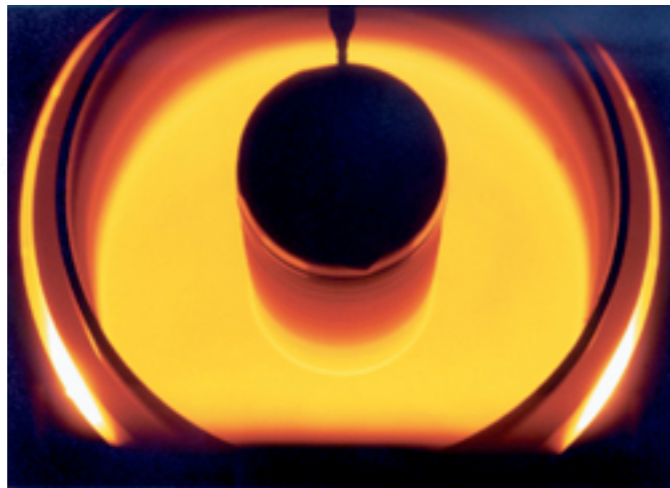


crystallization
of molten silicon

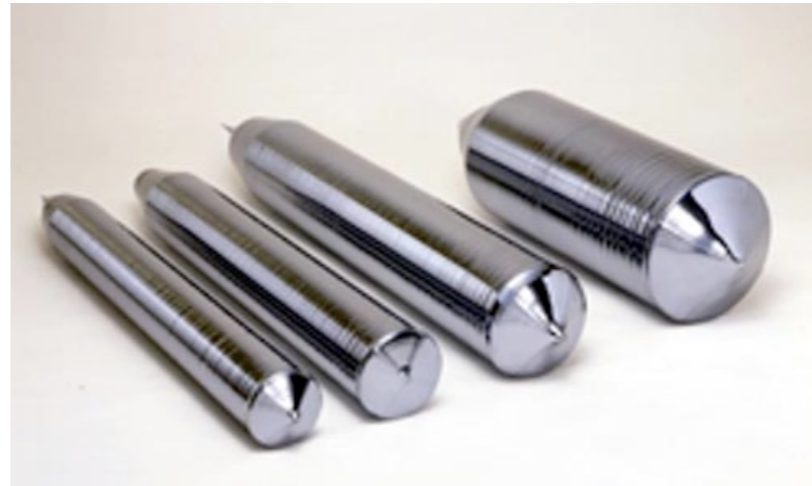


silicon ingots

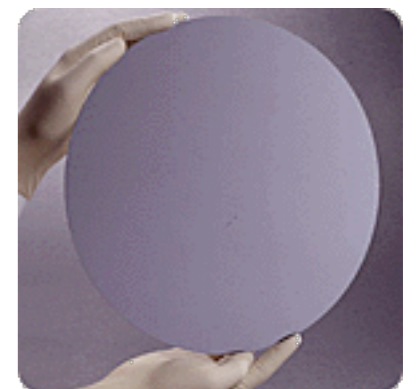



wafer

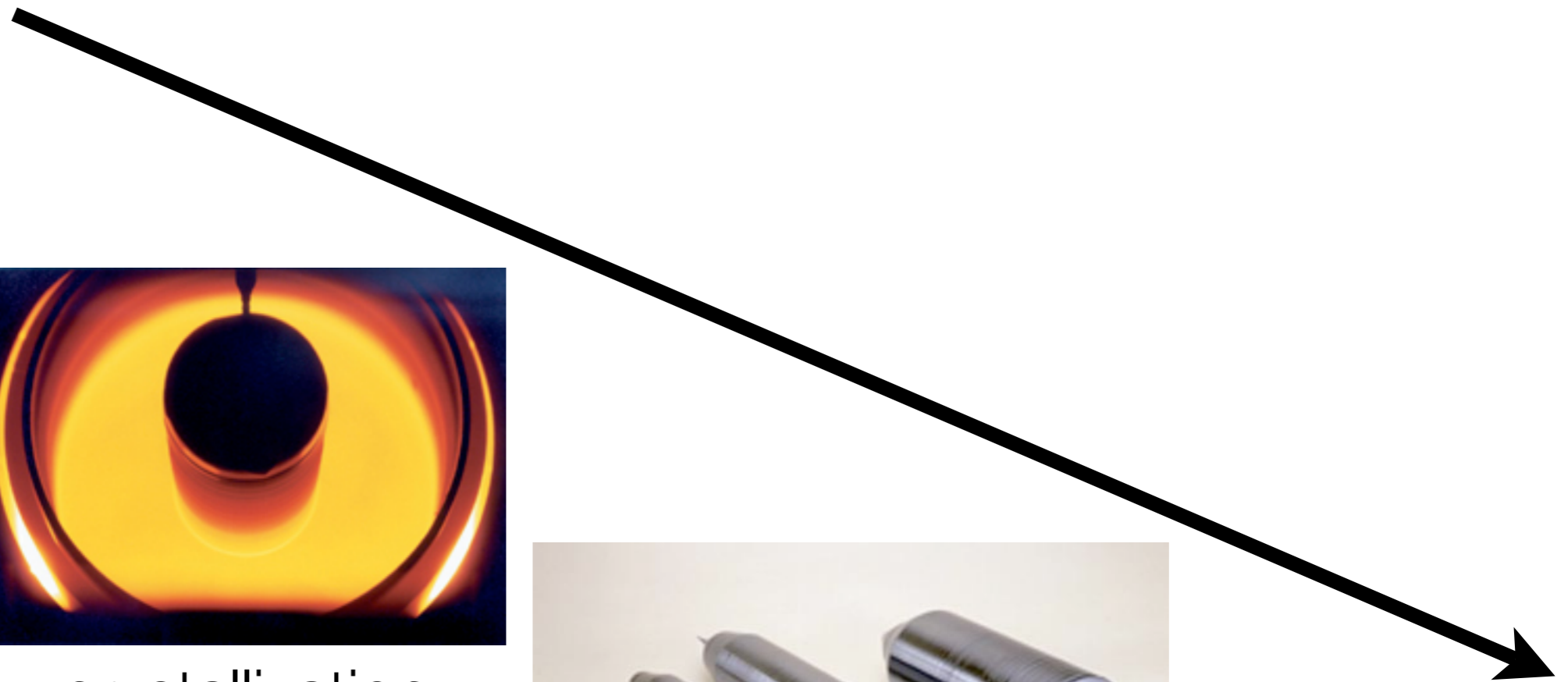


Integrated circuit fabrication 2

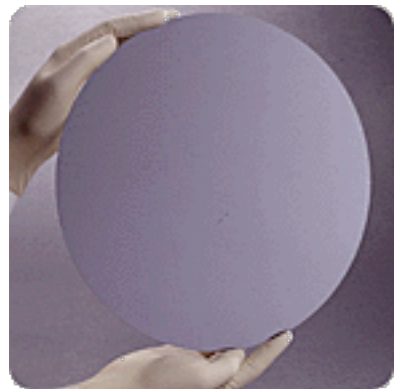


wafer

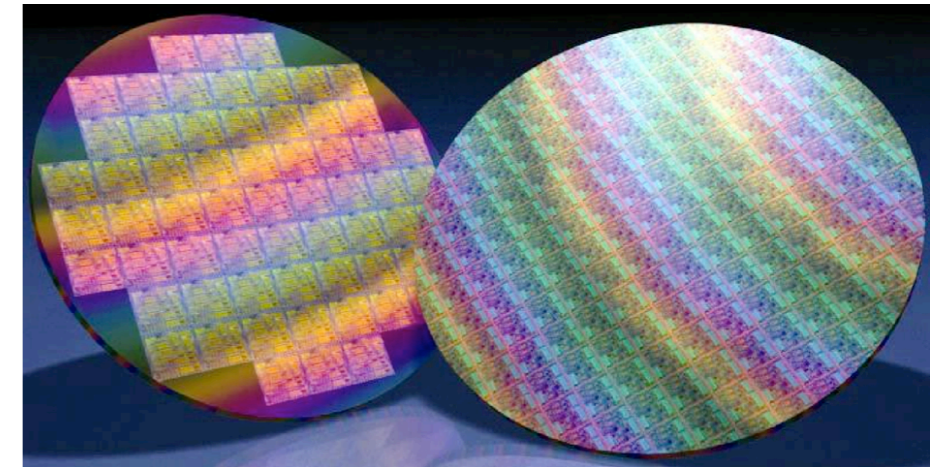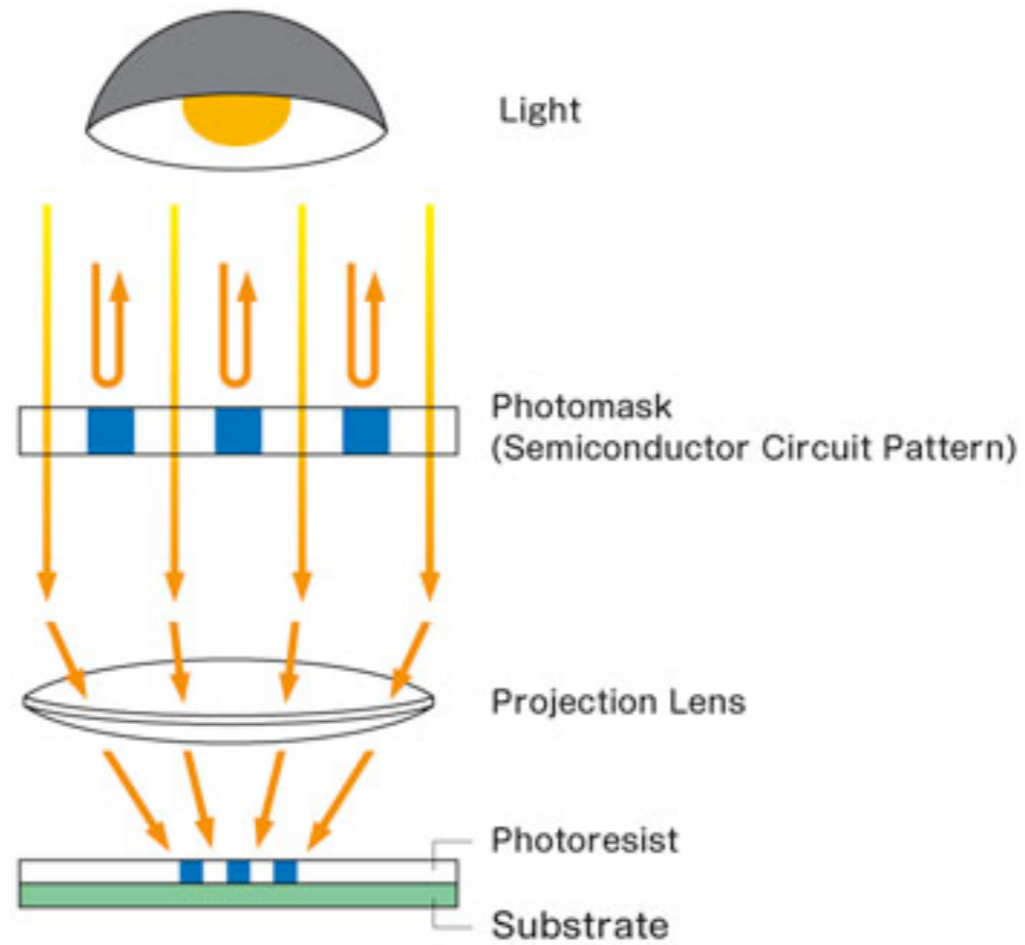


processed wafer

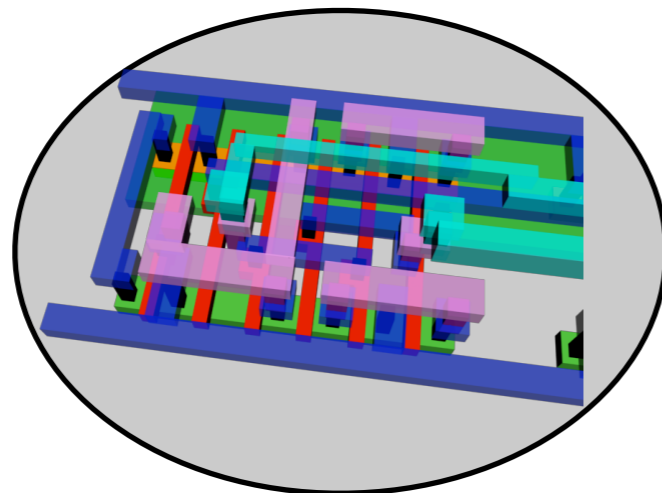


Integrated circuit fabrication 3

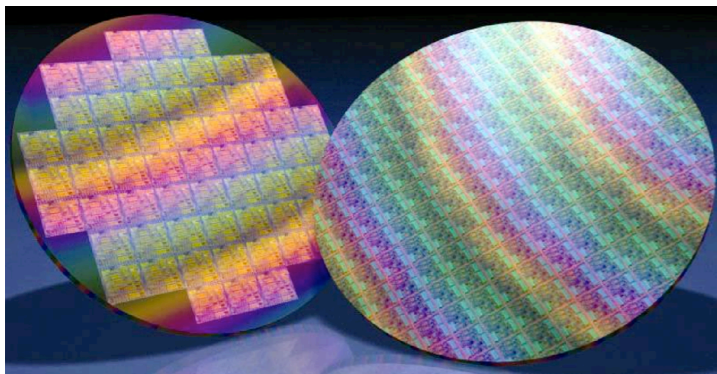

processed wafer

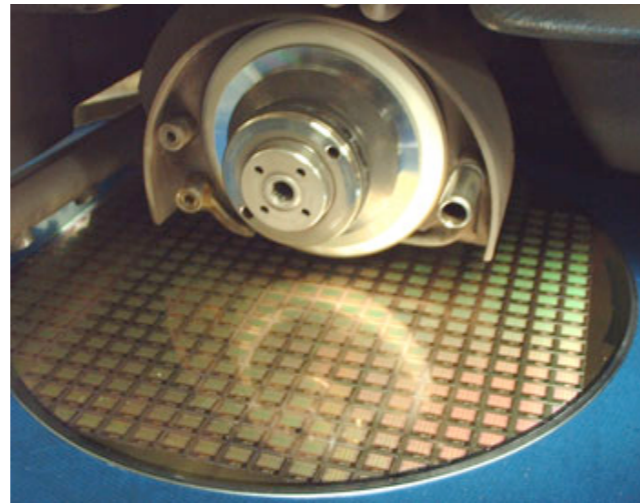


dicing

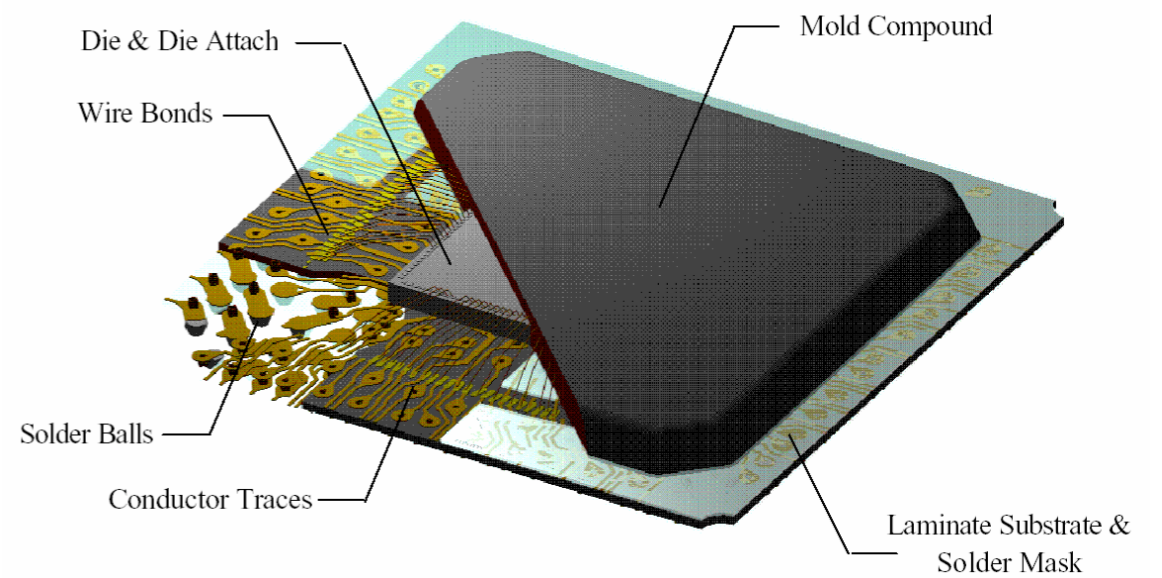

packaging

Integrated circuit fabrication 4

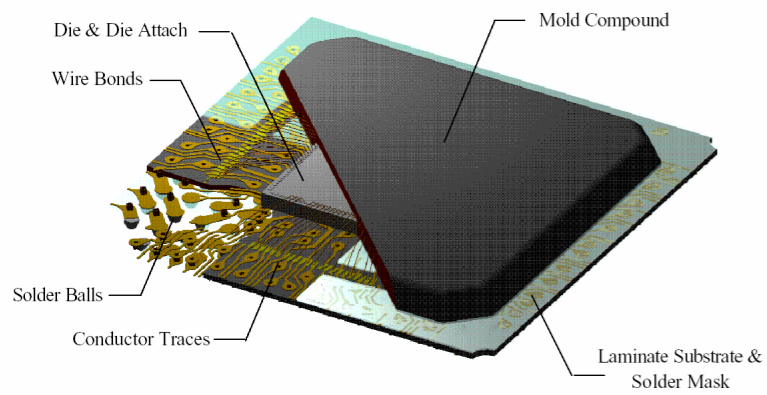

packaged die



test



A more detailed tutorial on integrated circuit fabrication:

<http://www.necel.com/fab/en/flow.html>

Next class: more boolean algebra, duals
