

CSEE 3827: Fundamentals of Computer Systems

Lecture 4 & 5

February 2 & 4, 2009

Martha Kim

martha@cs.columbia.edu

Standard forms (redux)

Product and sum terms

- Product term: logical AND of literals (e.g., $X\bar{Y}Z$)
- Sum term: logical OR of literals (e.g., $A + \bar{B} + C$)

Minterms

A	B	C	minterm	
0	0	0	m0	$\bar{A}\bar{B}\bar{C}$
0	0	1	m1	$\bar{A}\bar{B}C$
0	1	0	m2	$\bar{A}B\bar{C}$
0	1	1	m3	$\bar{A}BC$
1	0	0	m4	$A\bar{B}\bar{C}$
1	0	1	m5	$A\bar{B}C$
1	1	0	m6	$AB\bar{C}$
1	1	1	m7	ABC

- A product term in which all variables appear once, either complemented or uncomplemented.
- Each minterm evaluates to 1 for exactly one variable assignment, 0 for all others.
- Denoted by mX where X corresponds to the variable assignment for which $mX = 1$.

Sum of minterms form

- The logical OR of all minterms for which $F = 1$.

A	B	C	minterm	F
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$	0
0	0	1	m1 $\bar{A}\bar{B}C$	1
0	1	0	m2 $\bar{A}B\bar{C}$	1
0	1	1	m3 $\bar{A}BC$	1
1	0	0	m4 $A\bar{B}\bar{C}$	0
1	0	1	m5 $A\bar{B}C$	0
1	1	0	m6 $AB\bar{C}$	0
1	1	1	m7 ABC	0

$$\begin{aligned}F &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC \\ &= m1 + m2 + m3 \\ &= \sum m(1,2,3)\end{aligned}$$

Sum of minterms form (2)

- The logical OR of all minterms for which $F = 1$.

A	B	C	minterm	F	m0	m1	m2	m3	m4	m5	m6	m7
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$	0	1	0	+	0	+	0	0	0
0	0	1	m1 $\bar{A}\bar{B}C$	1	0	1	+	0	+	0	0	0
0	1	0	m2 $\bar{A}B\bar{C}$	1	0	0	+	1	+	0	0	0
0	1	1	m3 $\bar{A}BC$	1	0	0	+	0	+	1	0	0
1	0	0	m4 $A\bar{B}\bar{C}$	0	0	0	+	0	+	0	1	0
1	0	1	m5 $A\bar{B}C$	0	0	0	+	0	+	0	0	1
1	1	0	m6 $AB\bar{C}$	0	0	0	+	0	+	0	0	1
1	1	1	m7 ABC	0	0	0	+	0	+	0	0	1

Sum of minterms form (3)

- What is \bar{F} in sum of minterms form?

A	B	C	minterm	F
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$	0
0	0	1	m1 $\bar{A}\bar{B}C$	1
0	1	0	m2 $\bar{A}B\bar{C}$	1
0	1	1	m3 $\bar{A}BC$	1
1	0	0	m4 $A\bar{B}\bar{C}$	0
1	0	1	m5 $A\bar{B}C$	0
1	1	0	m6 $AB\bar{C}$	0
1	1	1	m7 ABC	0

Sum of minterms form (4)

- What is $A(\bar{B}+C)$ in sum of minterms form?

Maxterms

A	B	C	maxterm	
0	0	0	M0	$A+B+C$
0	0	1	M1	$A+B+\bar{C}$
0	1	0	M2	$A+\bar{B}+C$
0	1	1	M3	$A+\bar{B}+\bar{C}$
1	0	0	M4	$\bar{A}+B+C$
1	0	1	M5	$\bar{A}+B+\bar{C}$
1	1	0	M6	$\bar{A}+\bar{B}+C$
1	1	1	M7	$\bar{A}+\bar{B}+\bar{C}$

- A sum term in which all variables appear once, either complemented or uncomplemented.
- Each maxterm evaluates to 0 for exactly one variable assignment, 1 for all others.
- Denoted by MX where X corresponds to the variable assignment for which $MX = 0$.

Relationship between minterms and maxterms

- Minterms and maxterms with the same subscripts are complements.

$$\overline{mX} = MX$$

Product of maxterms form

- The logical AND of all maxterms for which $F = 0$.

A	B	C	maxterm	F
0	0	0	M0 $A+B+C$	0
0	0	1	M1 $A+B+\bar{C}$	1
0	1	0	M2 $A+\bar{B}+C$	1
0	1	1	M3 $A+\bar{B}+\bar{C}$	1
1	0	0	M4 $\bar{A}+B+C$	0
1	0	1	M5 $\bar{A}+B+\bar{C}$	0
1	1	0	M6 $\bar{A}+\bar{B}+C$	0
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$	0

$$\begin{aligned} F &= (A+B+C) (\bar{A}+B+C) (\bar{A}+B+\bar{C}) (\bar{A}+\bar{B}+C) (\bar{A}+\bar{B}+\bar{C}) \\ &= (M0) (M4) (M5) (M6) (M7) \\ &= \prod M(0,4,5,6,7) \end{aligned}$$

Product of maxterms form (2)

- The logical AND of all maxterms for which $F = 0$.

A	B	C	maxterm	F	M0	M1	M2	M3	M4	M5	M6	M7
0	0	0	M0 $A+B+C$	0	0	1	1	1	1	1	1	1
0	0	1	M1 $A+B+\bar{C}$	1	1	0	1	1	1	1	1	1
0	1	0	M2 $A+\bar{B}+C$	1	1	1	0	1	1	1	1	1
0	1	1	M3 $A+\bar{B}+\bar{C}$	1	1	1	1	0	1	1	1	1
1	0	0	M4 $\bar{A}+B+C$	0	1	1	1	1	0	1	1	1
1	0	1	M5 $\bar{A}+B+\bar{C}$	0	1	1	1	1	1	0	1	1
1	1	0	M6 $\bar{A}+\bar{B}+C$	0	1	1	1	1	1	1	0	1
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$	0	1	1	1	1	1	1	1	0

Product of maxterms form (3)

- What is \bar{F} in product of maxterms form?

A	B	C		maxterm	F
0	0	0	M0	$A+B+C$	0
0	0	1	M1	$A+B+\bar{C}$	1
0	1	0	M2	$A+\bar{B}+C$	1
0	1	1	M3	$A+\bar{B}+\bar{C}$	1
1	0	0	M4	$\bar{A}+B+C$	0
1	0	1	M5	$\bar{A}+B+\bar{C}$	0
1	1	0	M6	$\bar{A}+\bar{B}+C$	0
1	1	1	M7	$\bar{A}+\bar{B}+\bar{C}$	0

Summary of forms

	F	\bar{F}
Sum of minterms	$\sum m(F = 1)$	$\sum m(F = 0)$
Product of maxterms	$\prod M(F = 0)$	$\prod M(F = 1)$

POS & SOP


- Sum of products (SOP): OR of ANDs

$$\text{e.g., } F = \bar{Y} + \bar{X}Y\bar{Z} + XY$$

- Product of sums (POS): AND of ORs

$$\text{e.g., } G = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

Relations between standard forms

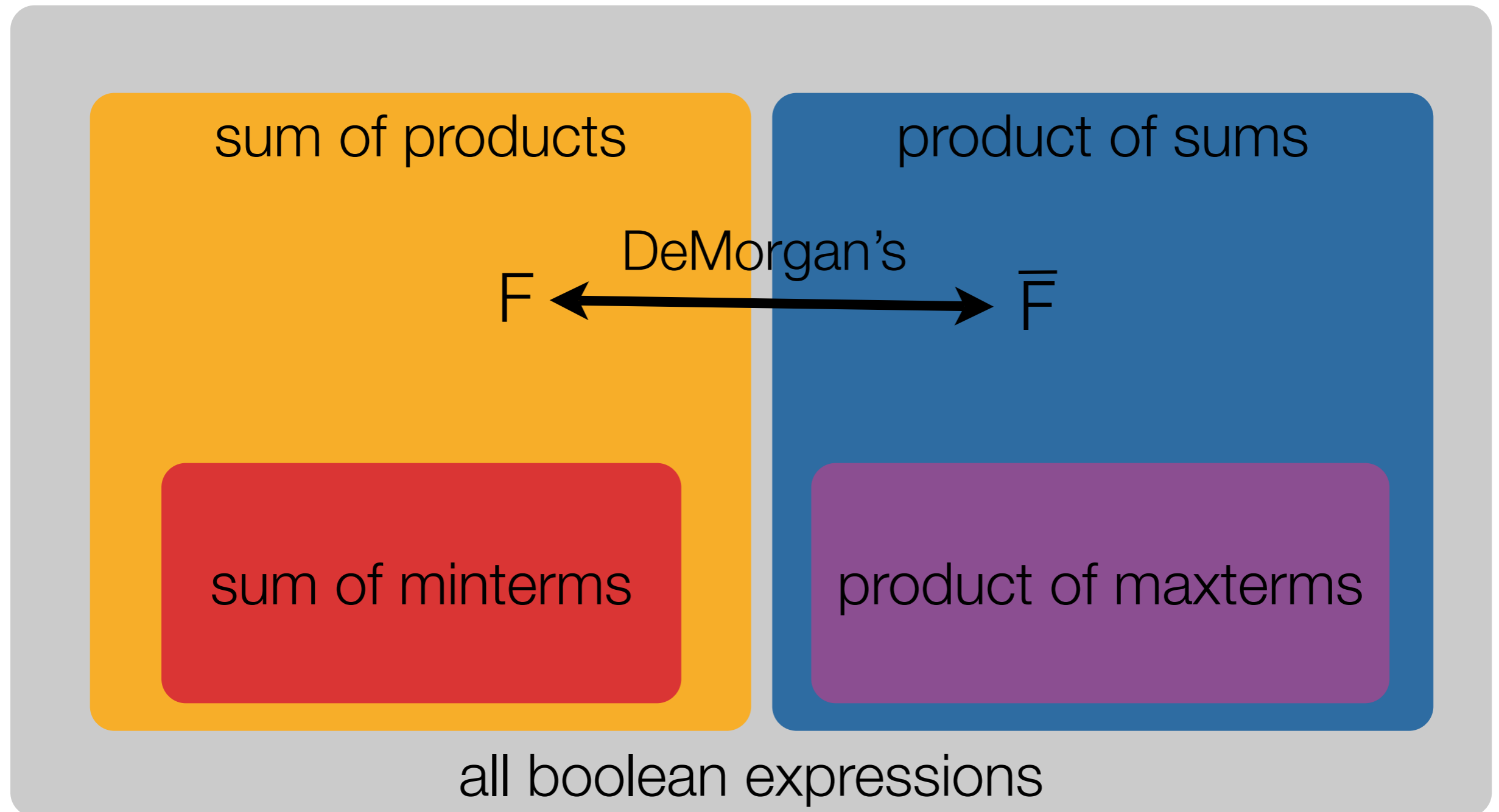

Expression simplification / circuit optimization

Cost criteria

- Literal cost: the number of literals in an expression
- Gate-input cost: the literal cost + all terms with more than one literal + (optionally) the number of distinct, complemented single literals

Roughly proportional to the number of transistors and wires in an AND/OR/NOT circuits. Does not apply, to more complex gates, for example XOR.

	Literal cost	Gate-input cost
$G = \bar{A}\bar{B}\bar{C}\bar{D} + ABCD$	8	$8 + 2 + (4)$
$G = (\bar{A}+B)(\bar{B}+C)(\bar{C}+D)(\bar{D}+A)$	8	$8 + 4 + (4)$

Karnaugh maps

- All functions can be expressed with a map
- There is one square in the map for each minterm in a function's truth table

X	Y	F
0	0	m0
0	1	m1
1	0	m2
1	1	m3

		Y	
		0	1
X	0	m0 $\overline{X}\overline{Y}$	m1 $\overline{X}Y$
	1	m2 $X\overline{Y}$	m3 XY

Karnaugh maps express functions

- Fill out table with value of a function

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	1

		Y	
		0	1
X	0	0	1
	1	1	1

Simplification using a k-map

- Whenever two squares share an edge and both are 1, those two terms can be combined to form a single term with one less variable

		Y	0	1
X	0		0	1
	1		1	1

$$F = \bar{X}Y + X\bar{Y} + XY$$

		Y	0	1
X	0		0	1
	1		1	1

$$F = Y + X\bar{Y}$$

		Y	0	1
X	0		0	1
	1		1	1


$$F = X + \bar{X}Y$$

		Y	0	1
X	0		0	1
	1		1	1

$$F = X + Y$$

Simplification using a k-map (2)

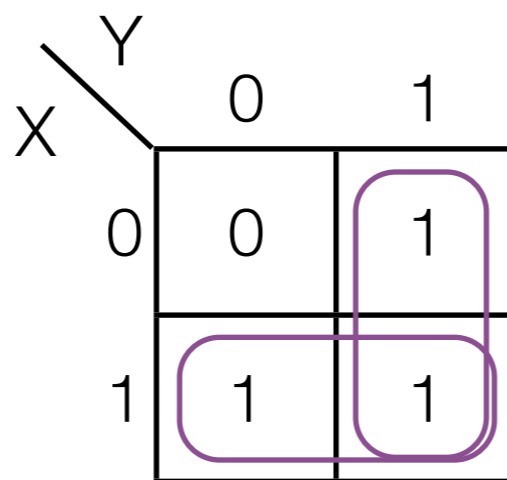
- Circle contiguous groups of 1s (circle sizes must be a power of 2)
- There is a correspondence between circles on a k-map and terms in a function expression
- The bigger the circle, the simpler the term
- Add circles (and terms) until all 1s on the k-map are circled



$$F = X + Y$$

Karnaugh maps: terminology

- A term is an **implicant** if it has the value 1 for all minterms (corresponds to any circled groups of 1, 2, 4, etc. 1s on a k-map)
- A term is a **prime implicant** if the removal of any literal makes it no longer an implicant (corresponds to circles that cannot be made any larger)
- If a minterm is included in only one prime implicant, that implicant is called an **essential prime implicant** (corresponds to any circle that is the only one to cover a 1 on a k-map)

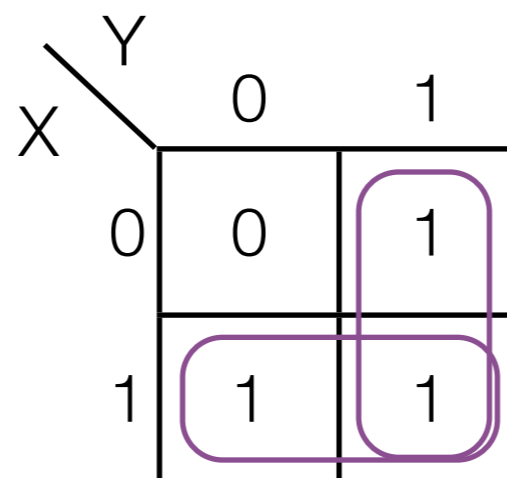


$$F = X + Y$$

Karnaugh-map example

X	Y	F
0	0	1
0	1	1
1	0	0
1	1	0


3-variable Karnaugh maps

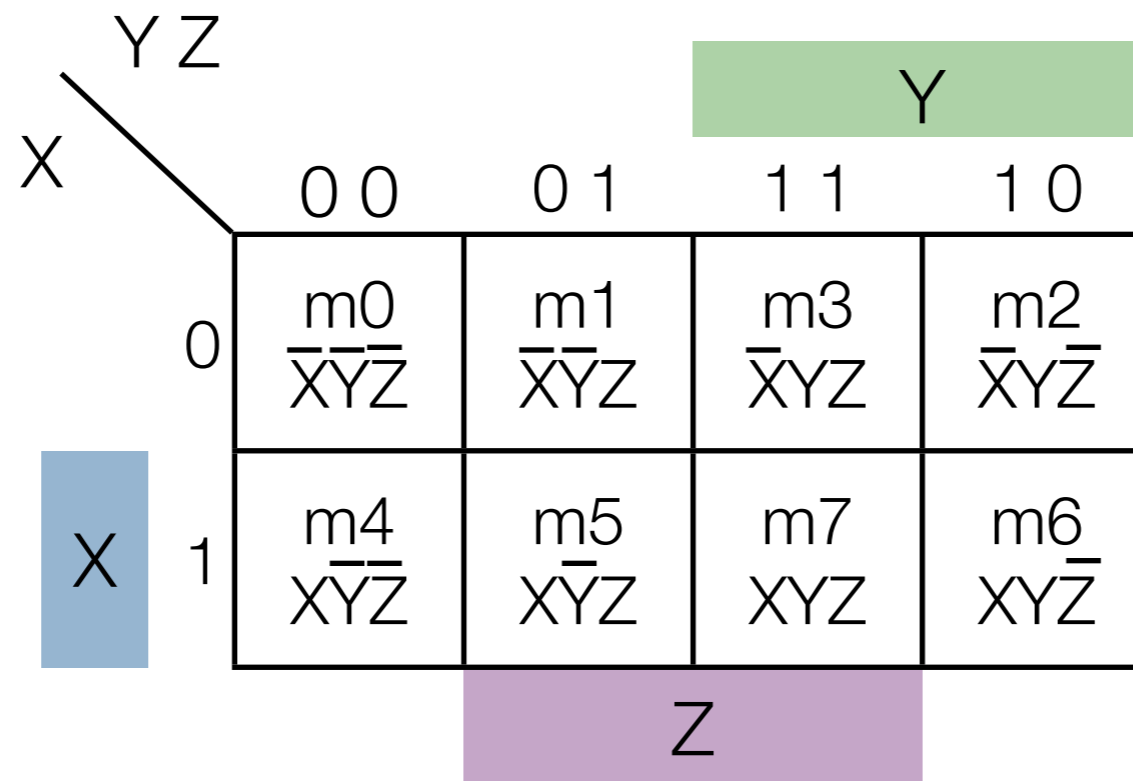- Use gray ordering on edges with multiple variables
- Gray encoding: order of values such that only one bit changes at a time
- Two minterms are considered adjacent if they differ in only one variable (this means maps wrap)




3-variable Karnaugh maps (2)

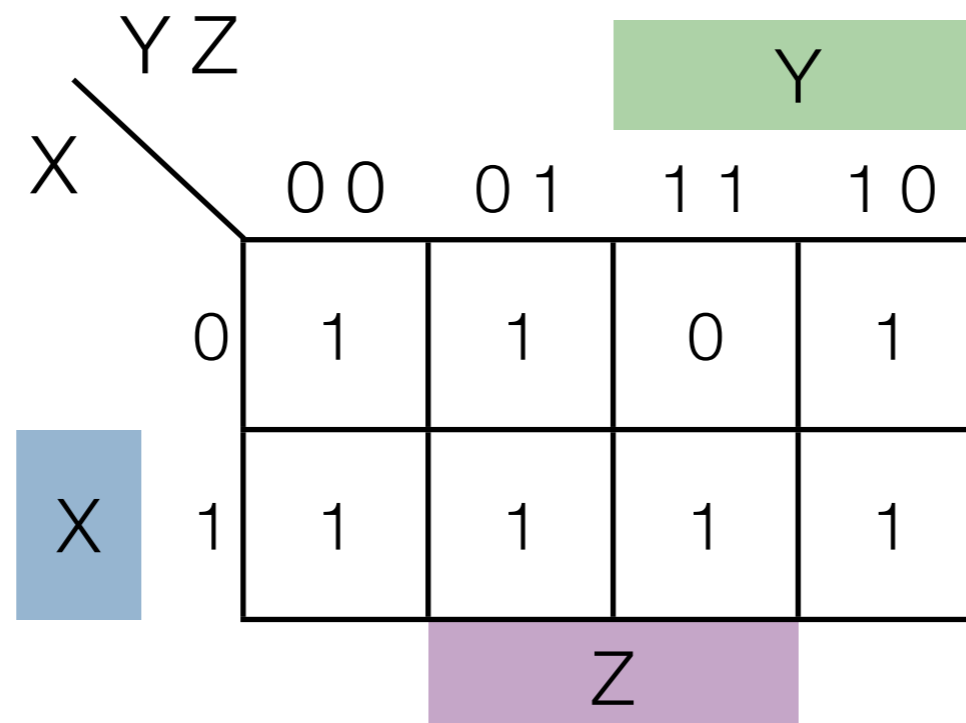- List all all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?




4-variable Karnaugh maps

- Extension of 3-variable maps

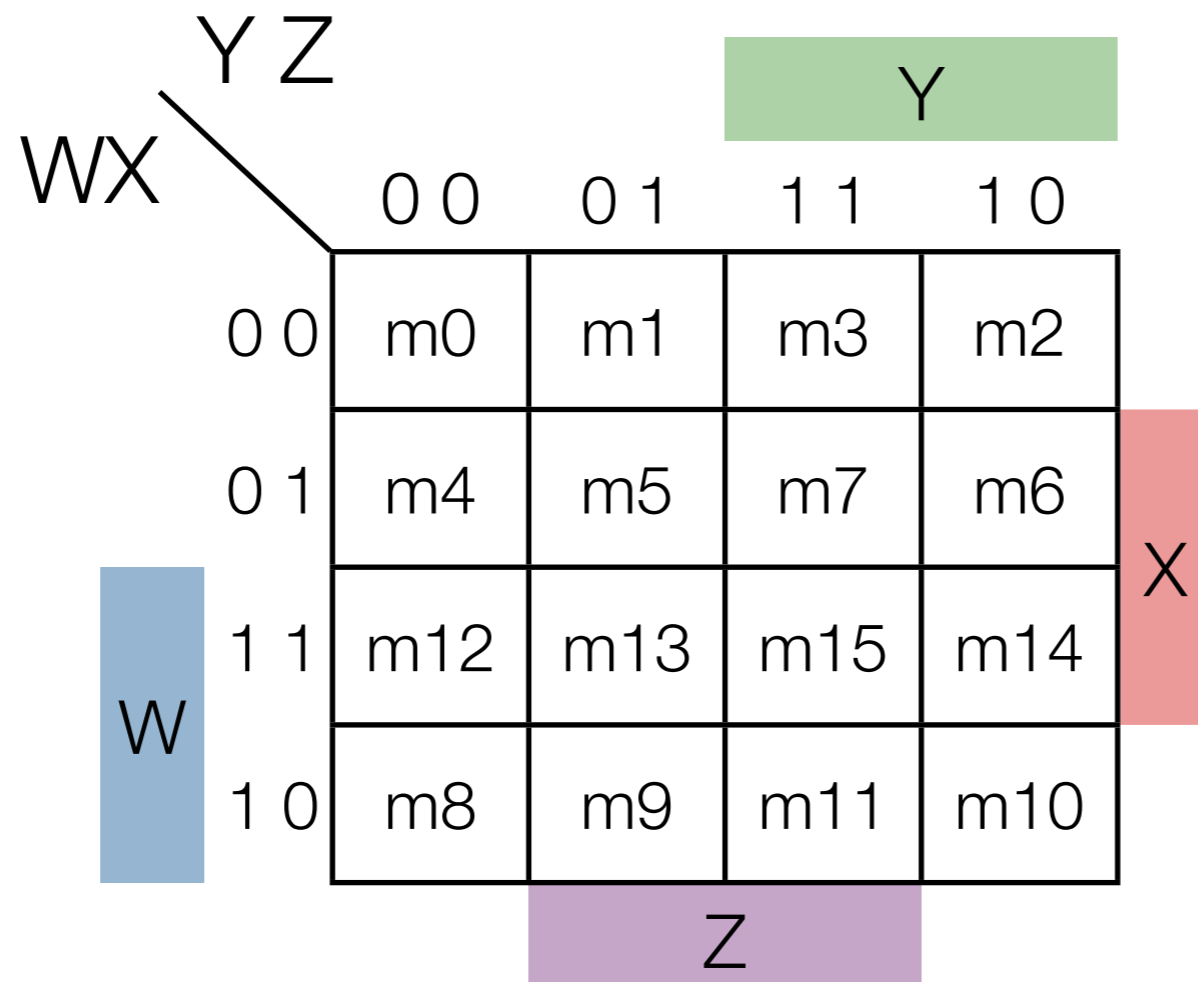


4-variable Karnaugh maps (2)

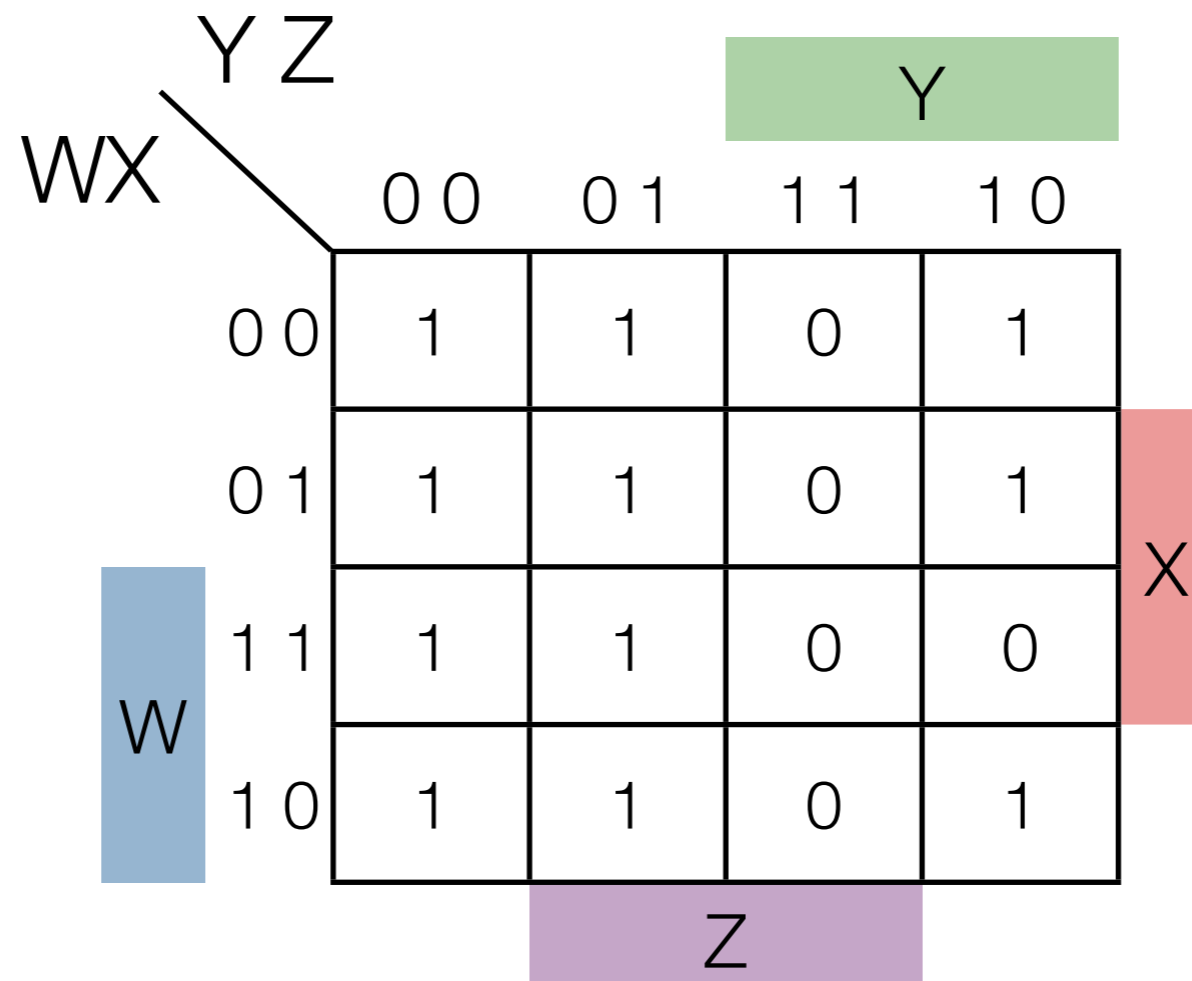- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?




4-variable Karnaugh maps (3)

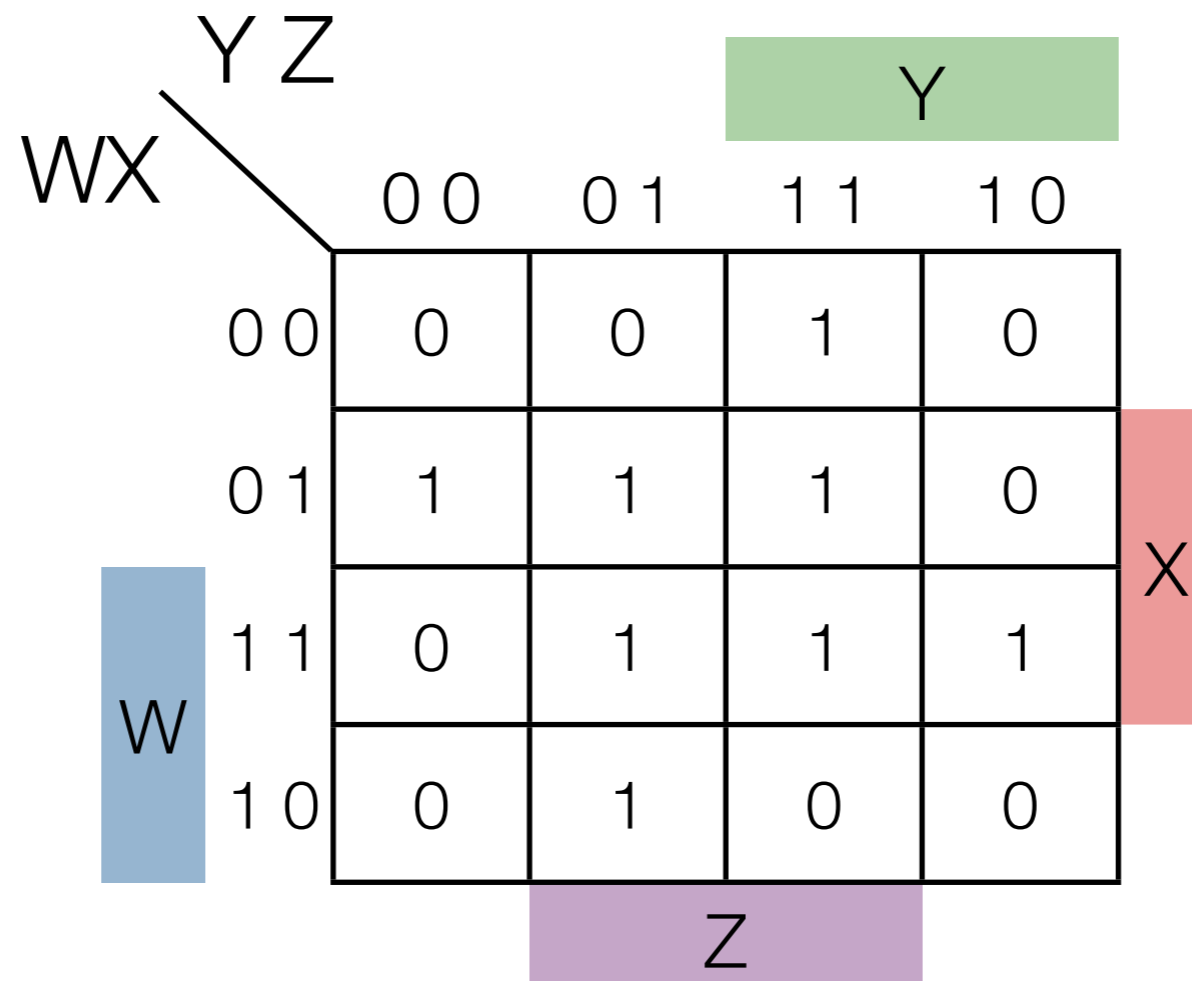
- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?



5-variable Karnaugh maps

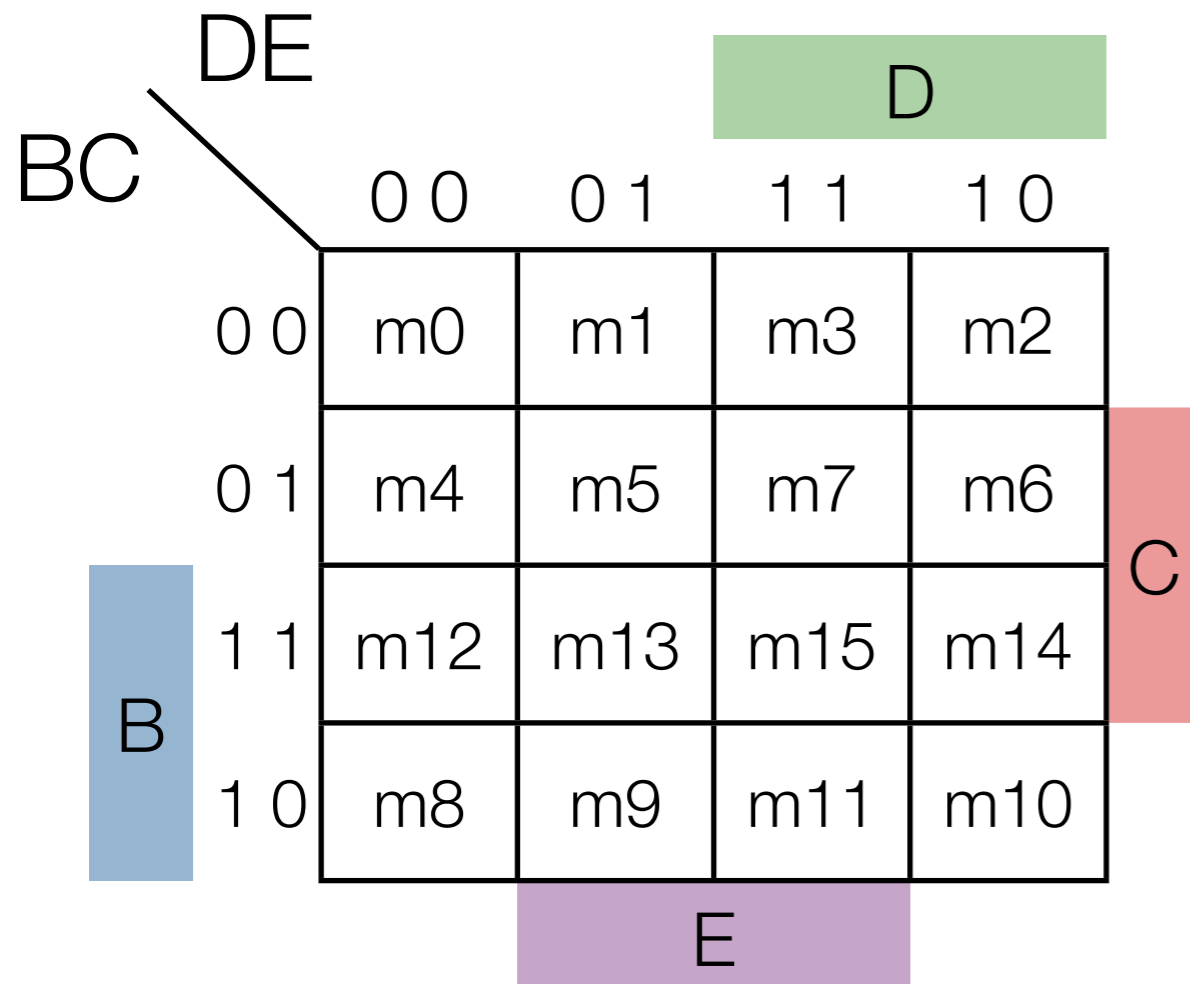


$A = 0$

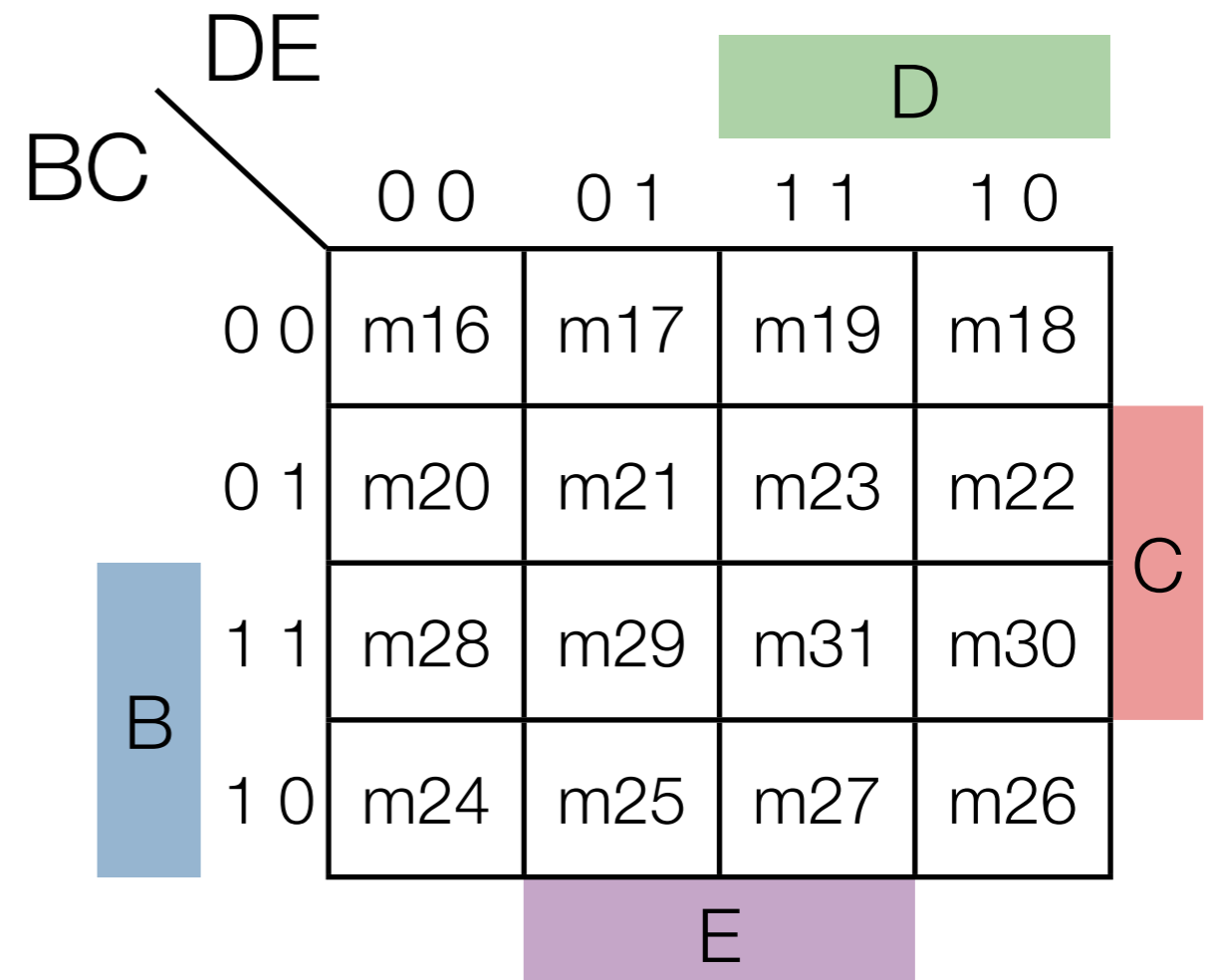


$A = 1$

5-variable Karnaugh map (2)

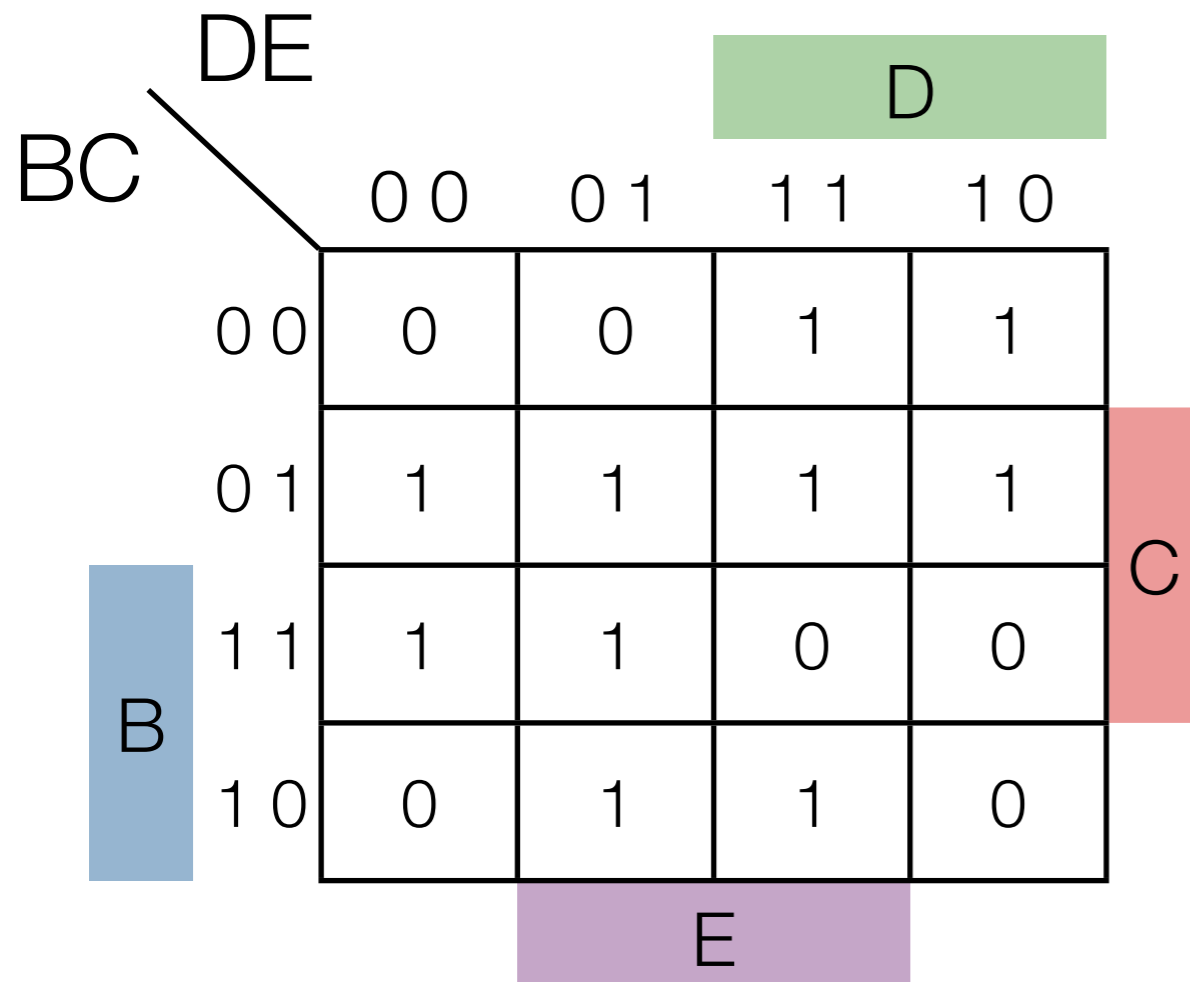- What is a simplified expression for this function?



$A = 0$

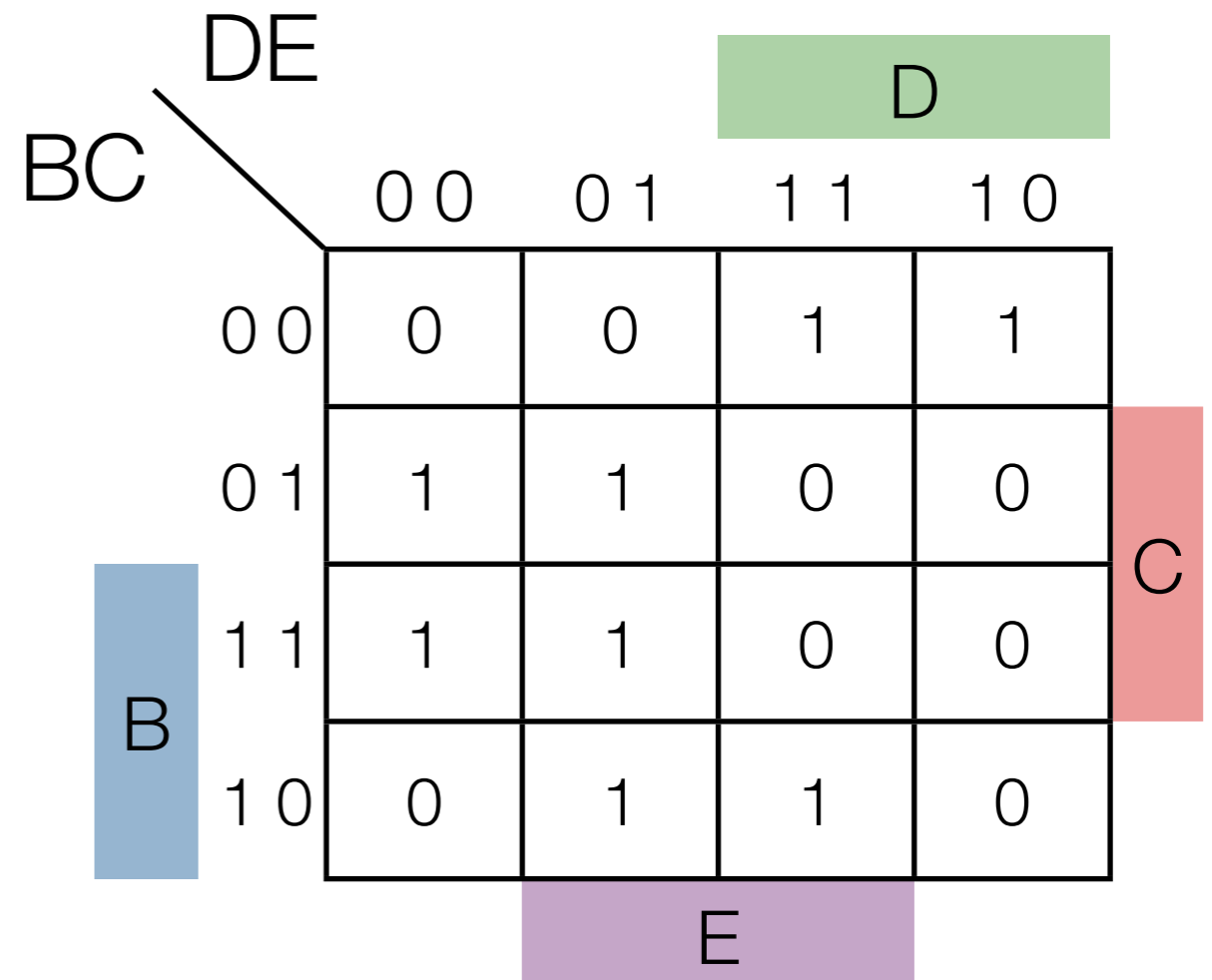

$A = 1$


Design example : 2-bit multiplier

a1	a0	b1	b0	z3	z2	z1	z0
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				


K-Maps: Complements, POS, don't care conditions

Finding \bar{F}

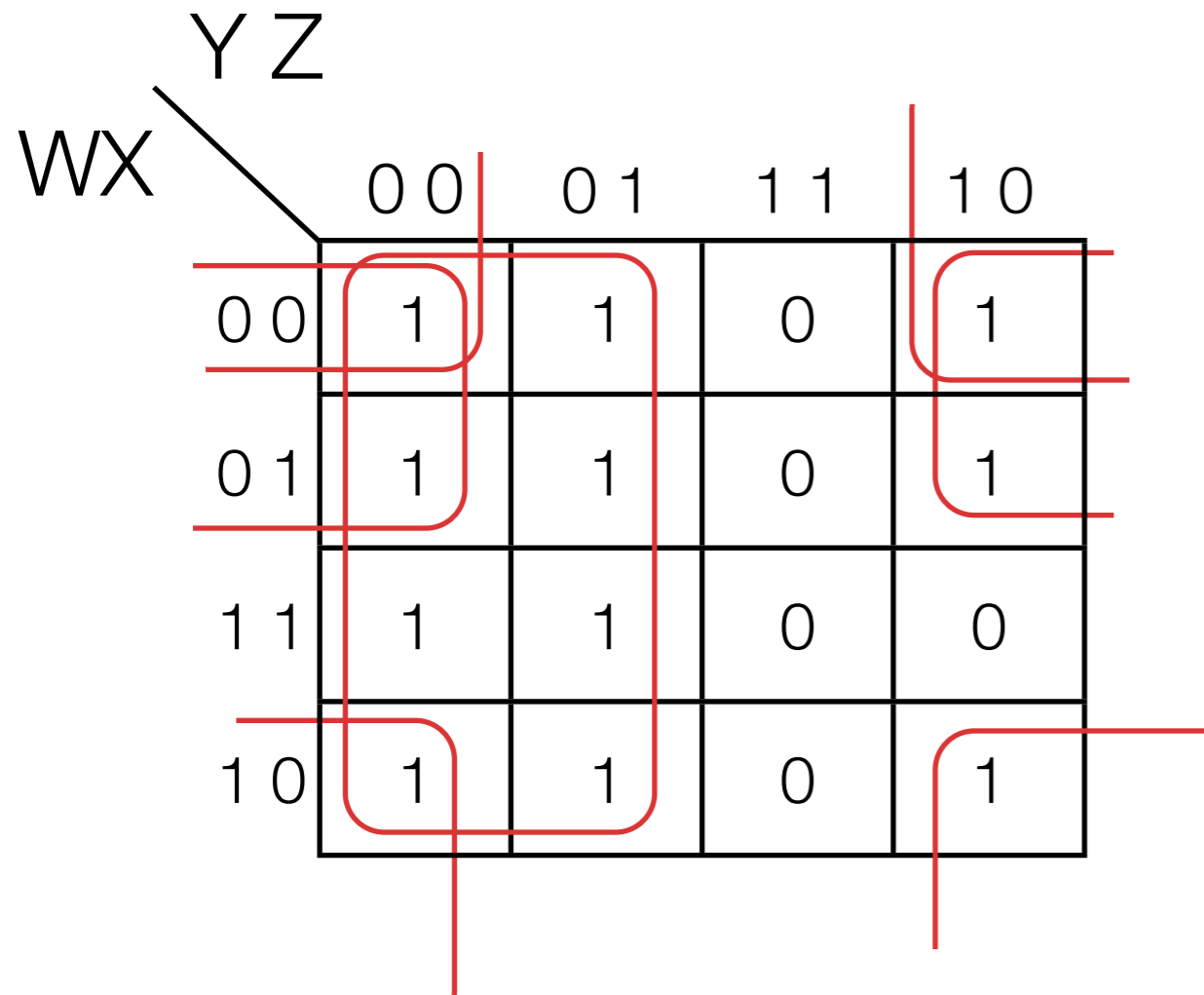- Find prime implicants corresponding to the 0s on a k-map


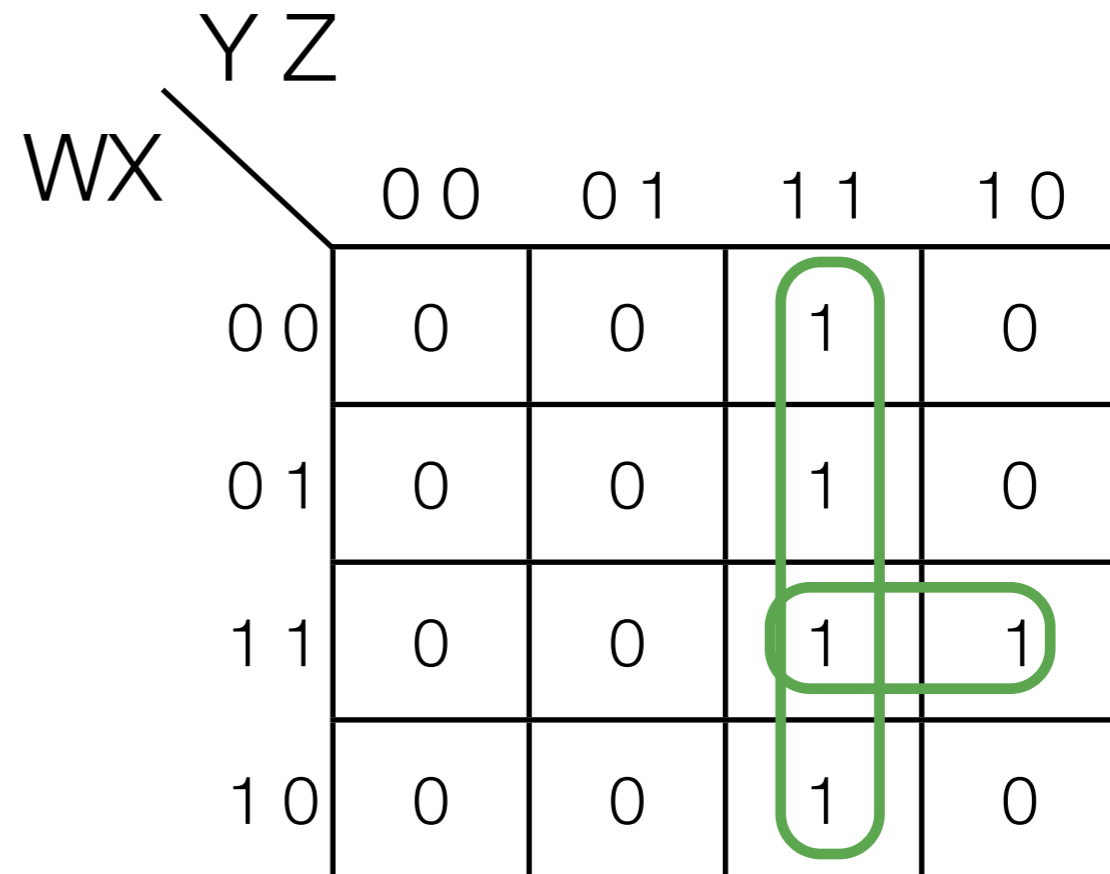
$$F = \bar{Y} + \bar{X}\bar{Z} + \bar{W}\bar{Z}$$



$$\bar{F} = YZ + WXY$$

POS expressions from a k-map

- Find \bar{F} as SOP and then apply DeMorgan's

WX \ YZ		YZ			
		00	01	11	10
WX	00	1	1	0	1
	01	1	0	0	0
	11	1	0	0	0
	10	1	1	0	1

$$\bar{F} = YZ + XZ + YX$$

DeMorgan's

$$F = (\bar{Y} + \bar{Z})(\bar{Z} + \bar{X})(\bar{Y} + \bar{X})$$

Optimized standard forms Example

- M&K 2-26 (b)
- Find optimized versions of F as SOP and as POS:

$$F(W,X,Y,Z) = \sum m(3,4,9,15)$$

$$d(W,X,Y,Z) = \sum m(0,1,2,5,10,14)$$

Don't care conditions

- There are circumstances in which the value of an output doesn't matter

- For example, in that 2-bit multiplier, what if there were only 3 bits for the product and one bit to indicate an overflow situation?

- Don't care situations are denoted by "x" in a truth table and in Karnaugh maps.

- Can also be expressed in minterm form:

$$z2 = \sum m(10, 11, 14)$$

$$d = \sum m(15)$$

- During minimization can be treated as either a 1 or a 0

a1	a0	b1	b0	o	z2	z1	z0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	x	x	x

Don't care example

- M&K 2-24 (a)
- Optimize this function:

$$F(A,B,C,D) = \sum m(0,1,7,13,15)$$

$$d(A,B,C,D) = \sum m(2,6,8,9,10)$$

Glitches and hazards

- Glitch: an unintended change in circuit output
- Hazard: the hardware structures that cause a glitch to occur
- Caused by multiple path delays through a circuit
- Example: $\bar{A}\bar{B} + BC$
- Avoidance
 - Synchronous design (coming later)
 - Extra implicants

Next week: multibit outputs and standard circuits
