


MLO:

A Multi-Level Optimizer For Burst Mode Asynchronous Controllers

Walter Dearing

Steven Nowick

 Computer Science Department
Columbia University



This work was supported by NSF ITR Award No. NSF-CCR-0086036 and
by an Initiatives in Science and Engineering (ISE) grant from
Columbia University (from the Office of the Executive Vice President for Research)



MLO: Access Information

- Accessible on the web from:
<http://www1.cs.columbia.edu/~nowick/asynctools>
- Initial Release
 - One version – for Linux Distributions
- Includes
 - Complete Tutorial
 - Documentation
 - Examples
- Tool requires Python interpreter to run:
<http://www.python.org/download/>
- Consult README for MLO installation information




Outline

- Introduction to MLO (Multi-Level Optimizer)
- Overview of features
- Example of features
- Example of gate networks produced
- Built-in verifier
- Brief tutorial


Introduction to MLO

- **Introduction to MLO (Multi-Level Optimizer)** ←

 - Overview of features
- Example of features
- Example of gate networks produced
- Built-in verifier
- Brief tutorial




Introduction to MLO

 


- MLO is an integrated **post-processing** (i.e. backend) tool for Minimalist.
- Targeted to **multi-level logic**.
 - In contrast, Minimalist currently is targeted to two-level logic.
- Designed to work on **combinational hazard-free logic** for Burst Mode controllers.
 - Uses “hazard-non-increasing” transforms.
- Output of MLO is Verilog.
- MLO is a standalone tool running from the Linux shell **outside of Minimalist.**

Introduction to MLO

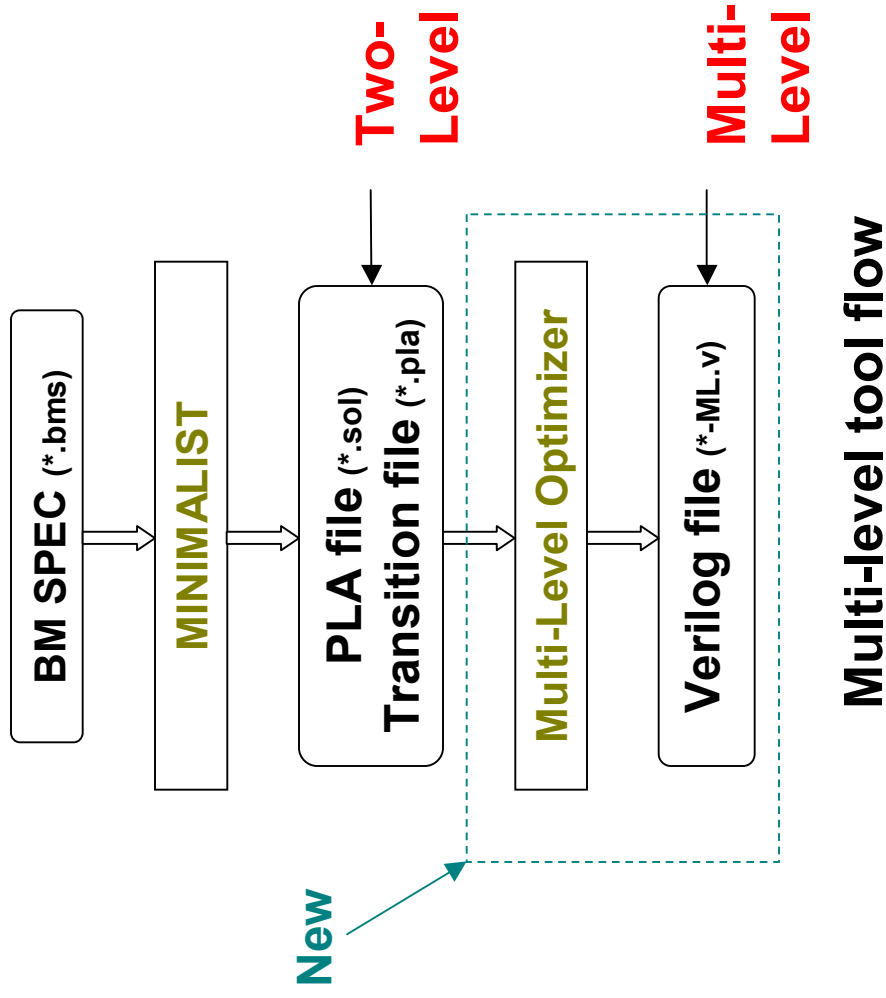


Overviews of features

 - Introduction to MLO (Multi-Level Optimizer)
- **Overview of features** ←
- Example of features
- Example of gate networks produced
- Built-in verifier
- Brief tutorial




Feature Set – Overview

 

MLO has many features which are orthogonal and can be used together.

1. **Gate fan-in limitation**
2. **Negative-logic**
3. **Critical Event Optimizer (CEO)**
 - Two modes
 - a) **Automated**
 - b) **User-specified**


Feature Set – Goal of CEO

 

Goal of CEO is to reduce the **critical path** of **critical events**.

- **Critical events** are defined as a transition of a primary output in response to an input transition
- Done by moving critical inputs closer to the primary output.
- Intention is for critical inputs to travel through the circuit as fast a possible.

 Feature Set – CEO Mode 1 - Automated Mode



CEO defaults to automated mode if no user input specified.

- Tool automatically optimizes **likely critical paths**.
- Focuses optimizations on **primary input-to-output paths** involved in **dynamic transitions**.
 - (i.e. $0 \rightarrow 1 / 1 \rightarrow 0$)

Feature Set – CEO Mode 2 - User-Specified Critical Events



User can specify details for CEO to use.


- User may know which primary input(s) are important to critical primary output.
- Done by defining a **critical transition & input/output pair** at the Burst-Mode spec level.
- For particular outputs specified during transition, user **overrides** automated mode.
 - Consider the situation on the next slide where user specifies input & outputs off specific arcs.

Feature Set – CEO Mode 2 - User-Specified Critical Events



User-Specified Critical Arcs Highlighted in Red

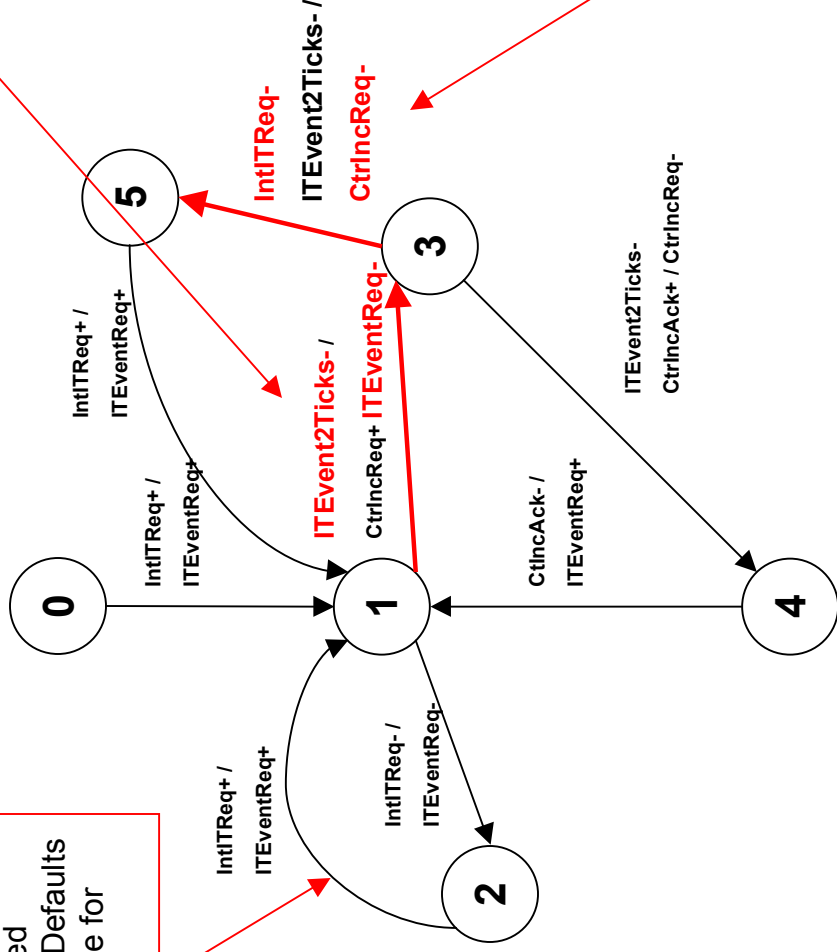Case 1: Non colored arc. User-Specified nothing is critical. Defaults to automated mode for every output.



Case 2: Some outputs colored, some outputs not. Both user-specified data and automated approaches are used to determine criticality. **ITEventReq** will use user-specified data to determine criticality. **CtrlncReq** will default to automated mode to determine criticality.

Case 3: Every output is colored. Automated approach is never used. **IntITReq-** is critical with respect to **CtrlncReq-**, while **ITEvent2Ticks-** is NOT critical to **CtrlncReq-**.




Example of features

- Introduction to MLO (Multi-Level Optimizer)
- Overview of features
- **Example of features** ←
- Example of gate networks produced
- Built-in verifier
- Brief tutorial



Feature Set - Initial Two-Level Implementation (before applying MLO)

 The next four slides present different MLO output examples. For each example, the starting circuit (input to MLO) is this circuit



Two-level Structure from Minimalist Output



Feature Set Example 2 - Negative Logic

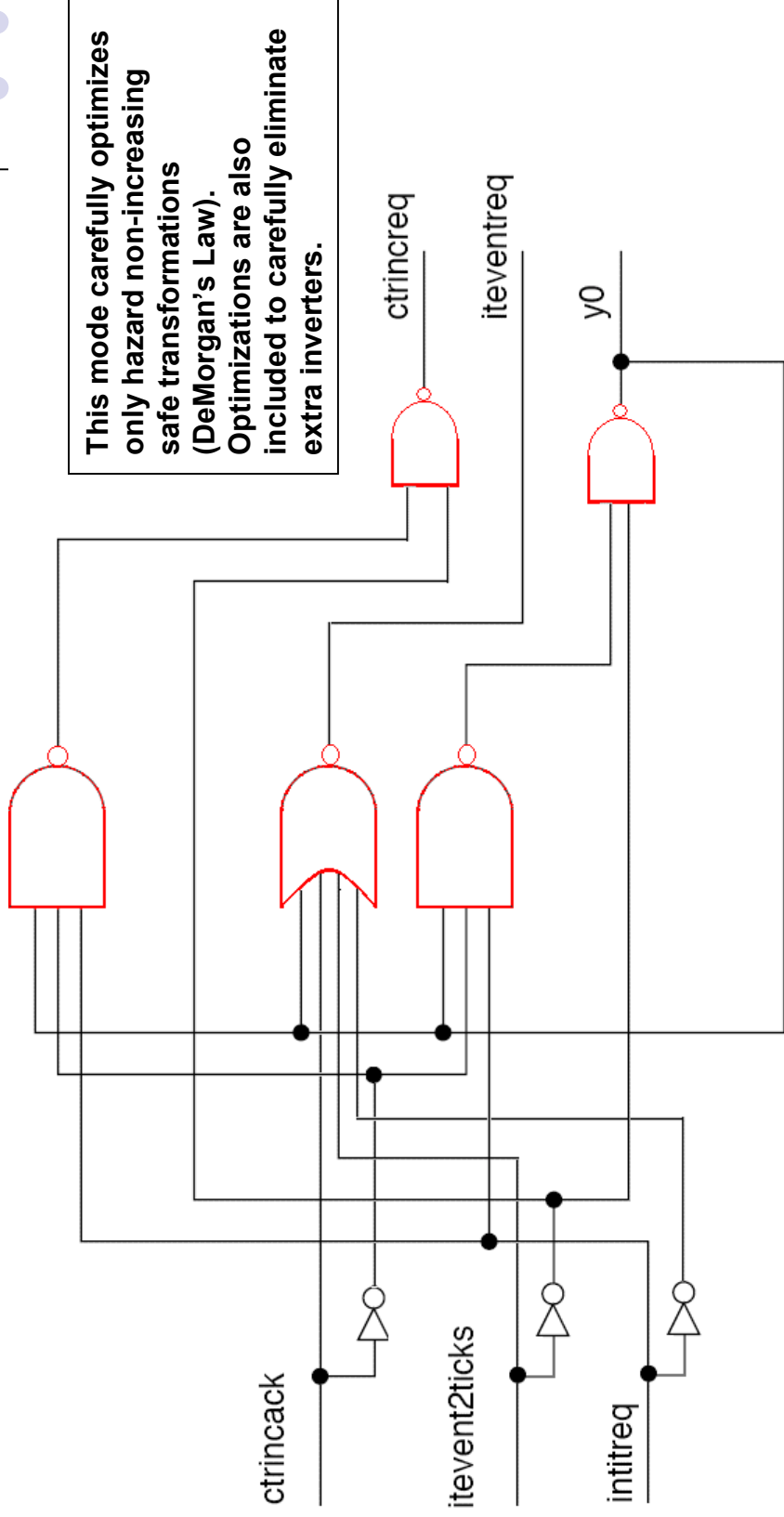 

This mode carefully optimizes only hazard non-increasing safe transformations (DeMorgan's Law). Optimizations are also included to carefully eliminate extra inverters.

Result of MLO: Multi-Level Circuit using **MLO Negative Logic**

Feature Set Example 3 - CEO

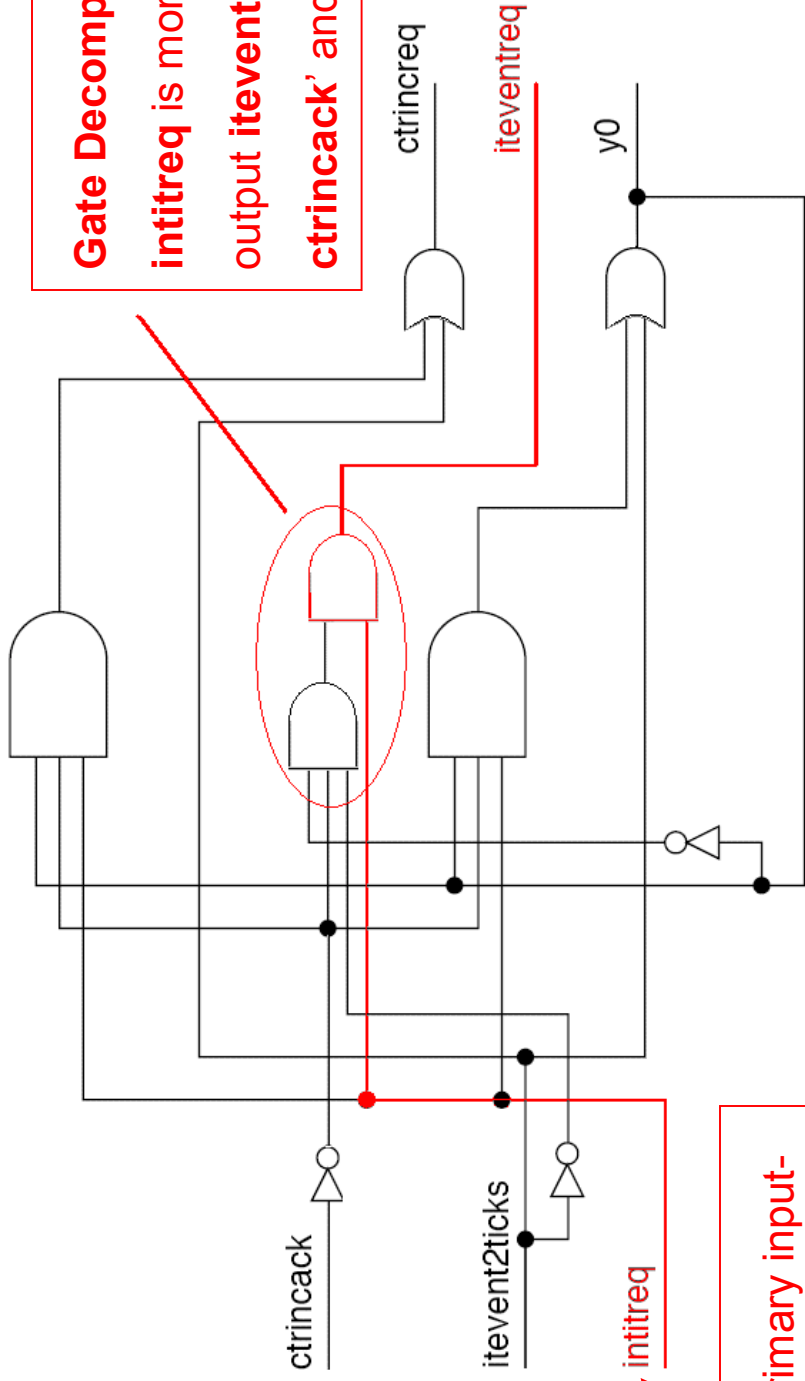
 


Gate Decomposed. Input **intitreq** is more critical to output **iteventreq** than **ctrincack'** and **y0'**

critical primary input-to-output path


Result of MLO: Multi-Level Circuit after MLO CEO is used

Feature Set Example 4 - Combined

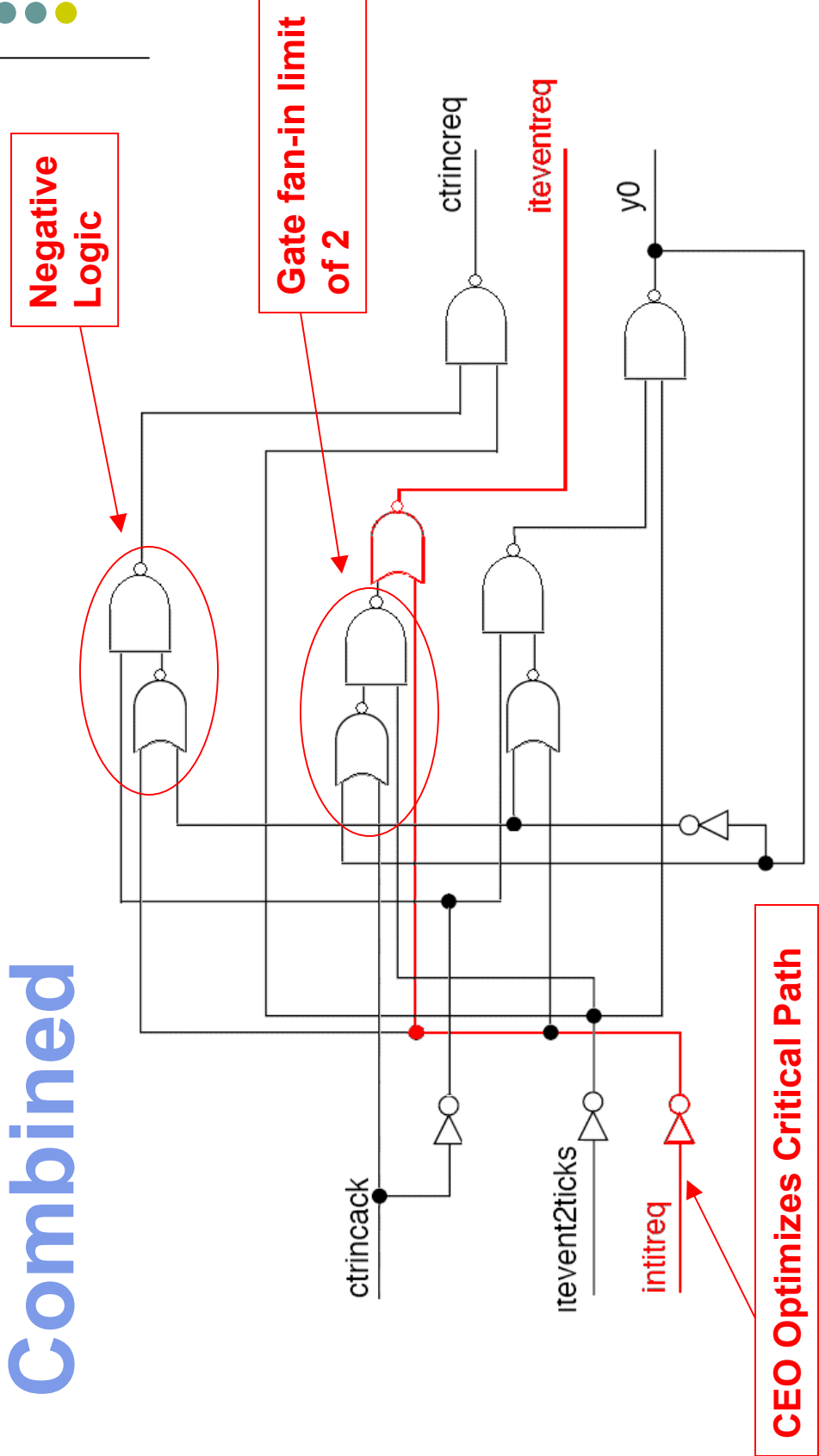 

Result of MLO: Multi-Level Circuit with **negative logic**, **AND gate fan-in limit of 2**, and **CEO**.

Example of gate networks produced

- Introduction to MLO (Multi-Level Optimizer)
- Overview of features
- Example of features
- **Example of gate networks produced** 
- Built-in verifier
- Brief tutorial






Gate Decomposition

- Gates can be decomposed in two ways
 - CEO – resulting network will be cascaded
 - Fan-in limitations – resulting network will be balanced
- Network can be a mixture of two methods.
- Consider a 6 input AND gate....


Gate Decomposition - Cascaded

 

Gate is decomposed based on **priority difference of inputs**


Lowest Input Priority
(state variables only)

Highest Input Priority

 


Only used for CEO

Gate Decomposition – Balanced

 


Gate is decomposed strictly based on **fan-in limitation**

All Inputs have the same priority

 


Only used for gate fan-in limitation

Gate Decomposition – Mix

 

Gate is decomposed based on **both** difference in priority of inputs and fan-in limits

 Low Priority **Medium Priority** **High Priority**



Combination of **gate fan-in limitation** and **CEO**




Brief tutorial

- Introduction to MLO (Multi-Level Optimizer)
- Overview of features
- Example of features
- Example of gate networks produced
- **Built-in verifier** ←
- Brief tutorial


Built-in Verifier

 - A verifier is built into MLO.
- Verifies MLO output is **functionally correct** and **hazard free**
- Compares two-level structure (Minimalist output) to multi-level structure (MLO output).
- Verifies specific properties hold for each gate network in multi-level structure.
- Must be explicitly set using command line flag (not run by default)





Brief tutorial

- Introduction to MLO (Multi-Level Optimizer)
- Overview of features
- Example of features
- Example of gate networks produced
- Built-in verifier
- **Brief tutorial** 



Tutorial

- The spec file `hp-ir.bms` will be used during this tutorial.
- This can be found in the examples folder.
- Every command used in the tutorial is also described in the **tool help menu**.
 - To display general help menu
 - > `MLO.py --help`
 - To display user-specified critical event help menu
 - > `MLO.py --more_help`

Tutorial - Setup

Create the files needed for MLO to process

Step 1 – Create working directory

```
> mkdir MLO_tutorial
```

Step 2 – Copy spec file

```
> cp examples/hp-ir.bms  
MLO_tutorial/
```

Step 3 – Enter Directory


```
> cd MLO_tutorial
```

Step 4 – Create .pla & .sol files

```
> minimalist-speed hp-ir.bms  
single-output feedback
```

Step 5 – Verify files created
 
```
> Verify hp_IR-Fs.sol and hp_IR-  
Fs.pla has been created
```



Two-Level circuit from Minimalist

Assumes Minimalist is loaded and paths are set correctly!



Tutorial – Gate Fan-In Limitation

Implement circuit with gate fan-in limit of 2 for AND gates. This can be done using two different methods (results will be the same)

Method 1: Independently

Specify fan-in limit for AND gates only

Step 1 – Run MLO

```
> MLO.py -A 2 -d hp_IR-Fs.sol
```

Step 2 – View Results

```
> less hp_IR-Fs-ML.v
```

Step 3 – Verify Results

```
> Compare output with circuit on next page
```

Method 2: Globally

Specify fan-in limit for every gate type

Step 1 – Run MLO

```
> MLO.py -M 2 -d hp_IR-Fs.sol
```

Step 2 – View Results

```
> less hp_IR-Fs-ML.v
```

Step 3 – Verify Results

```
> Compare output with circuit on next page
```

Tutorial – Gate Fan-In Limitation

```
module hp_IR_Fs (intitreq, itevent2ticks, ctrincack, iteventreq, ctrincreq);
input intitreq, itevent2ticks, ctrincack;
output iteventreq, ctrincreq;

wire neg_ctrincack, neg_ctrincreq_i, neg_itevent2ticks, ctrincreq_i, ctrincreq, _i1;
wire _i2, _i3;
// Wires needed for multi-level
wire _i4, _i5, _i6;
// Feedback variables
assign ctrincreq_i = ctrincreq;

// Negative input literals
not (neg_ctrincack, ctrincack);
not (neg_ctrincreq_i, ctrincreq_i);
not (neg_itevent2ticks, itevent2ticks);

// First plane of logic
// -- Network implementing gate _i3 --
and (_i3, _i4, neg_ctrincack);
and (_i4, intitreq, ctrincreq_i);
// -- Network implementing gate _i2 --
assign _i2 = itevent2ticks;
// -- Network implementing gate _i1 --
and (_i1, _i5, _i6);
and (_i5, neg_ctrincack, neg_ctrincreq_i);
and (_i6, intitreq, neg_itevent2ticks);

// Second plane of logic
// -- Network implementing gate CtrIncReq --
or (ctrincreq, _i3, _i2);
// -- Network implementing gate ITevenReq --
assign iteventreq = _i1;

endmodule
```

MLO Output:

2 AND gates have been decomposed based on fan-in limit of 2.

Tutorial – Negative Logic

Implement circuit using negative logic.

Step 1 – Run MLO


```
> MLO.py -n -d hp_IR-Fs.sol
```

Step 2 – View Results

```
> less hp_IR-Fs-ML.v
```

Step 3 – Verify Results
 
```
> Compare output with  
circuit on next page
```



MLO Result: Multi-Level Circuit using negative logic only

Tutorial – Negative Logic

```
module hp_IR_Fs (intitreq, itevent2ticks, ctrincack, iteventreq, ctrincreq);
input intitreq, itevent2ticks, ctrincack;
output iteventreq, ctrincreq;

wire neg__i2, neg_ctrincack, neg_intitreq, ctrincreq_i, ctrincreq, _i1;
wire _i2, _i3;
// Wires needed for multi-level
wire neg__i3;
// Feedback variables
assign ctrincreq_i = ctrincreq;


// Negative input literals
not (neg__i2, _i2);
not (neg_ctrincack, ctrincack);
not (neg_intitreq, intitreq);

// First plane of logic
// -- Network implementing gate neg__i3 --
nand (neg__i3, neg_ctrincack, intitreq, ctrincreq_i);
// -- Network implementing gate _i2 --
assign _i2 = itevent2ticks;
// -- Network implementing gate _i1 --
nor (_i1, ctrincack, ctrincreq_i, neg_intitreq, itevent2ticks);

// Second plane of logic
// -- Network implementing gate CtrIncReq --
nand (ctrincreq, neg__i3, neg__i2);
// -- Network implementing gate ITEventReq --
assign iteventreq = _i1;
endmodule
```

MLO Output:
Only NOT/NOR/NAND gates used.

 Tutorial – CEO Critical Event Optimizer (Automated Mode)



Run MLO using defaults (CEO on, no gate fan-in limits, and no negative logic).

Step 1 – Run MLO

```
> MLO.py hp_IR-Fs.sol
```


Step 2 – View Results

```
> less hp_IR-Fs-ML.v
```

Step 3 – Verify Results

```
> Compare output with circuit on next page
```

 No switch selected: default is CEO in auto mode



critical primary input-to-output path

Multi-Level circuit after **CEO** is used

Tutorial – CEO

```
module hp_IR_Fs (intitreq, itevent2ticks, ctrincack, iteventreq, ctrincreq);
input intitreq, itevent2ticks, ctrincack;
output iteventreq, ctrincreq;

wire neg_ctrincack, neg_itevent2ticks, neg_ctrincreq_i, ctrincreq, _i1;
wire _i2, _i3;
// Wires needed for multi-level
wire _i4;
// Feedback variables
assign ctrincreq_i = ctrincreq;

// Negative input literals
not (neg_ctrincack, ctrincack);
not (neg_itevent2ticks, itevent2ticks);
not (neg_ctrincreq_i, ctrincreq_i);

// First plane of logic
// -- Network implementing gate _i3 --
and (_i3, neg_ctrincack, intitreq, ctrincreq_i);
// -- Network implementing gate _i2 --
assign _i2 = itevent2ticks;
// -- Network implementing gate _i1 --
and (_i1, intitreq, _i4);
and (_i4, neg_itevent2ticks, neg_ctrincack, neg_ctrincreq_i);

// Second plane of logic
// -- Network implementing gate CtrIncReq --
or (ctrincreq, _i2, _i3);
// -- Network implementing gate IEventReq --
assign iteventreq = _i1;
endmodule
```

MLO Output:

Gate Decomposed. Input intitreq is more critical to output iteventreq than neg_ctrincack and neg_ctrincreq_i

Tutorial – Features Mix

Features can be mixed and matched. This example does not utilize CEO, but it does target negative logic circuit and limits fan-in to 2.

Step 1 – Run MLO


```
> MLO.py -d -n -R 2 -N 2 hp_IR-Fs.sol
```

Step 2 – View Results

```
> less hp_IR-Fs-ML.v
```

Step 3 – Verify Results
 
> Compare output with circuit on next page



Tutorial – Features Mix

```
module hp_IR_Fs (intitreq, itevent2ticks, ctrincack, iteventreq, ctrincreq);
input intitreq, itevent2ticks, ctrincack;
output iteventreq, ctrincreq;


wire neg__i2, neg_ctrincack, neg_intitreq, neg_ctrincreq_i, neg_itevent2ticks, ctrincreq_i;
wire ctrincreq, _i1, _i2, _i3;
// Wires needed for multi-level
wire _i4, _i5, _i6, neg__i3;
// Feedback variables
assign ctrincreq_i = ctrincreq;
// Negative input literals
not (neg__i2, _i2);
not (neg_ctrincack, ctrincack);
not (neg_intitreq, intitreq);
not (neg_ctrincreq_i, ctrincreq_i);
not (neg_itevent2ticks, itevent2ticks);

// First plane of logic
// -- Network implementing gate neg__i3 --
nand (neg__i3, _i4, neg_ctrincack);
nor (_i4, neg_intitreq, neg_ctrincreq_i);
// -- Network implementing gate _i2 --
assign _i2 = itevent2ticks;
// -- Network implementing gate _i1 --
nor (_i1, _i5, _i6);
nand (_i5, neg_ctrincack, neg_ctrincreq_i);
nand (_i6, intitreq, neg_itevent2ticks);

// Second plane of logic
// -- Network implementing gate CtrIncReq --
nand (ctrincreq, neg__i3, neg__i2);
// -- Network implementing gate ITEventReq --
assign iteventreq = _i1;
endmodule
```


MLO Output:
Only NOT/NOR/NAND gates
used and fan-in limited to 2

 Tutorial – User-Specified Critical Events - Overview



- MLO originally needed only two files to run (*.pla and *.sol)
- To utilize User-Specified Critical Events, MLO now needs two additional files:
 1. state_info.txt
 2. *.bms spec-file

 Tutorial – User-Specified Critical Events – state_info.txt




State minimization data is needed to utilize User-Specified Critical Events

- This information is only found on standard output during run of Minimalist.
- Therefore new program **capture_min_data** is needed to redirect Minimalist output to **state_info.txt**
- Runs from linux shell
- Wrapper around Minimalist call
- Important to note that **capture_min_data** **only** works with single-run

Minimalist scripts. In other words, it doesn't work for script suites

 Tutorial – User-Specified Critical Events – state_info.txt



Syntax Rules:

1. `capture_min_data` simply precedes Minimalist call.
 - For example, if user wants to capture data of minimalist-area script using multi-output run type, the syntax would be

```
> capture_min_data minimalist-area hp-ir.bms multi-output
```
2. Syntax for Minimalist command line options are same as if `capture_min_data` was **not** being used.


Tutorial – User-Specified Critical Events – *.bms spec-file



Burst Mode Spec file has to be edited to specify critical events.

- Critical events will be specified by providing critical input/output pairs for specified transitions in the burst-mode specification.
- If all inputs are critical for output during transition, wildcard(“*”) can be used.
- No blank lines can surround any inserted user-specified critical comments(“; CRITICAL” statements) in the *.bms file.
- Comment must immediately precede the transition that it is describing.

 Tutorial – User-Specified Critical Events - *.bms spec-file



Syntax Rules (**red** comment):

1. To specify that the input CtrlIncAck+ is critical to CtrlIncReq- during transition from current state 3 to next state 4 (note that this is also saying that ITevent2Ticks is NOT critical):

```
;CRITICAL: CtrlIncAck+/CtrlIncReq-  
3 4 ITevent2Ticks- CtrlIncAck+ | CtrlIncReq-
```

2. To specify all inputs are critical to CtrlIncReq- from current state 3 to next state 5:

```
;CRITICAL: */CtrlIncReq-  
3 5 ITevent2Ticks- CtrlIncAck+ | CtrlIncReq-
```

3. Another way to specify all inputs are critical (same as Rule #2) to CtrlIncReq- during a transition from current state 3 to next state 5:

```
;CRITICAL: ITevent2Ticks-/CtrlIncReq-, CtrlIncAck+/CtrlIncReq-  
3 5 ITevent2Ticks- CtrlIncAck+ | CtrlIncReq-
```

4. If no input/outputs are marked critical, automated CEO is used. Automated CEO is used to rate criticality of ITevent2Ticks and CtrlIncAct with respect to CtrlIncReq:


```
3 5 ITevent2Ticks- CtrlIncAck+ | CtrlIncReq-
```

Tutorial – User-Specified Critical Events

Therefore, there are three steps to use User-Specified Critical Events

 1. Capture **output of Minimalist**.
 - Run Minimalist with `capture_min_data` to create `state_info.txt`
2. **Specify critical events** in spec file (*.bms).
 - Add `;CRITICAL...` statements
3. **Run MLO** with proper command line options.
 - Must use `-U` [`*.bms spec-file`] option.
 - Only have to specify `*.bms` and `*.sol` file, MLO assumes `state_info.txt` and `*.pla` are in same directory as `*.sol`.

Tutorial – User-Specified Critical Events: Complete Run



Specify User-Specified Critical Events

Step 1 – Capture Minimalist Output

```
> capture_min_data minimalist-speed hp-ir.bms single-output
```

Step 2 – Edit spec file

```
>emacs (or vi) hp-ir.bms
```

Step 3 – Add critical events to spec file (default auto mode will be used for other events)

```
> add line in red to file:
```

```
;CRITICAL: CtrIncAck+/CtrIncReq-
```

```
3      4      ITEvent2Ticks-      CtrIncAck+      |      CtrIncReq-
```

Step 4 – Run MLO

```
> MLO.py -U hp-ir.bms hp_IR-s.sol
```


Step 5 – View Results

```
> less hp_IR-s-ML.v
```

Step 6 – Verify Results

```
> Compare output with circuit on next page
```

Tutorial – User Defined Critical Events

 

```
module hp_IR_s (intitreq, itevent2ticks, ctrincack, iteventreq, ctrincreq);
input intitreq, itevent2ticks, ctrincack, ctrincreq;
output iteventreq, ctrincreq;
wire neg_ctrincack, neg_itevent2ticks, neg_y0_i, y0_i, y0, _i1;
wire _i2, _i3, _i4, _i5;
// Wires needed for multi-level
wire _i6, _i7;
// Feedback variables
assign y0_i = y0;
// Negative input literals
not (neg_ctrincack, ctrincack);
not (neg_itevent2ticks, itevent2ticks);
not (neg_y0_i, y0_i);
// First plane of logic
// -- Network implementing gate _i5 --
and (_i5, neg_ctrincack, _i6);
and (_i6, intitreq, y0_i);
// -- Network implementing gate _i4 --
assign _i4 = itevent2ticks;
// -- Network implementing gate _i3 --
and (_i3, intitreq, _i7);
and (_i7, neg_itevent2ticks, neg_ctrincack, neg_y0_i);
// -- Network implementing gate _i2 --
and (_i2, neg_ctrincack, intitreq, y0_i);
// -- Network implementing gate _i1 --
assign _i1 = itevent2ticks;
// Second plane of logic
// -- Network implementing gate CtrIncReq --
or (ctrincreq, _i5, _i4);
// -- Network implementing gate y0 --
or (y0, _i2, _i1);
// -- Network implementing gate ITEventReq --
assign iteventreq = _i3;
endmodule
```

Gate decomposed using fact that user-specified neg_ctrincack is critical to ctrincreq

Notice that Automated CEO is still used on outputs not specified by user

Tutorial – Verifier

Run MLO using with CEO and use the verifier to ensure output is functionally correct and hazard free

Step 1 – Run MLO

```
> MLO.py -V hp_IR-s.sol
```

Step 2 – Verify MLO output passes verifier (verify success message is printed)

```
> check standard output
```

If output passes built-in verifier, a success message will be printed to standard output.

Verification Results

Output has been verified - Everything OK.



Recap

- MLO uses Minimalist two-level logic output and produces an optimized multi-level circuit specified in Verilog.
- Tool has multiple features including negative logic implementations, critical-event optimizer, and gate fan-in limitations.