 


# Altera's Avalon Interface

Stephen A. Edwards

Columbia University


Spring 2025



- ▶ **Avalon Memory Mapped Host:**  
Initiates transactions (e.g., processor)  
Complex protocol requests access first
- ▶ **Avalon Memory Mapped Agent:**  
Responds to hosts (e.g., peripheral, memory)  
Simpler protocol: just responds

Also manager/subordinate, M/S,  
initiator/target, requester/responder  
See *Avalon Interface Specifications*

# The Simplest Agent Peripheral

 

Basically, "latch when I'm selected and written to."

## Agent Signals

For a 16-bit connection that spans 32 halfwords,


Agent	Avalon
← clk	Clock to Agent
← reset	Reset signal to Agent
← chipselect	Asserted when bus accesses Agent
⇐ address[4:0]	Register address (in words)
← read	Bus is reading from Agent
← write	Bus is writing to Agent
⇐ writedata[15:0]	Data from bus to Agent
⇐ byteenable[1:0]	Which bytes are being transferred
readdata[15:0] ⇒	Data from Agent to bus
irq →	Interrupt request to processor

All are optional, as are many others for, e.g., flow-control and burst transfers.

## In SystemVerilog

```
module myagent(input logic      clk,  
               input logic      reset,  
               input logic [7:0] writedata,  
               input logic      write,  
               input logic      chipselect,  
               input logic [2:0] address);
```

## Basic Agent Read Transfer

 


Bus cycle starts on rising clock edge

Data latched at next rising edge

Such a peripheral must be purely combinational

## Agent Read Transfer w/ 1 Wait State

 


Bus cycle starts on rising clock edge

Data latched two cycles later

Approach used for synchronous peripherals

## Basic Async. Agent Write Transfer

 


Bus cycle starts on rising clock edge

Data available by next rising edge

Peripheral may be synchronous, but must be fast
 
## Basic Async. Agent Write w/ 1 Wait State




Bus cycle starts on rising clock edge

Peripheral latches data two cycles later

For slower peripherals

# VGA on the DE1-SoC

 

# The Vga\_ball Peripheral

```
module vga_ball(input logic      clk,
                input logic      reset,
                input logic [7:0] writedata,
                input logic      write,
                input            chipselect,
                input logic [2:0] address,

                output logic [7:0] VGA_R, VGA_G, VGA_B,
                output logic      VGA_CLK, VGA_HS, VGA_VS,
                output logic      VGA_BLANK_n,
                output logic      VGA_SYNC_n);

    logic [10:0] hcount;
    logic [9:0]  vcount;

    logic [7:0] background_r, background_g, background_b;
    vga_counters counters(.clk50(clk), .*);
```

# Register Map

## Offset 7 ... 0 Meaning

0	Red	Red component of background color (0–255)
1	Green	Green component of background color (0–255)
2	Blue	Blue component of background color (0–255)

# The Vga\_ball Peripheral

```
always_ff @(posedge clk)
  if (reset) begin
    background_r <= 8'h0;
    background_g <= 8'h0;
    background_b <= 8'h80;
  end else if (chipselect && write)
    case (address)
      3'h0 : background_r <= writedata;
      3'h1 : background_g <= writedata;
      3'h2 : background_b <= writedata;
    endcase

always_comb begin
  {VGA_R, VGA_G, VGA_B} = {8'h0, 8'h0, 8'h0};
  if (VGA_BLANK_n )
    if (hcount[10:6] == 5'd3 && vcount[9:5] == 5'd3)
      {VGA_R, VGA_G, VGA_B} = {8'hff, 8'hff, 8'hff};
    else
      {VGA_R, VGA_G, VGA_B} = {background_r, background_g, background_b};
end
```